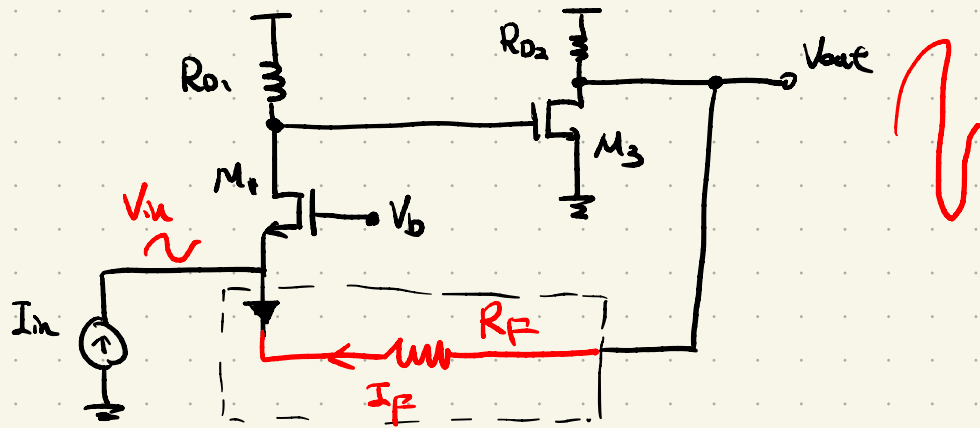


Lec 38

- Example of Voltage - Current Feedback
- Current - Voltage Feedback

Example



Observation:

- A good TIA has a low input imp.
 \Rightarrow a small input voltage
- A good TIA has a high gain
 \Rightarrow a large output voltage

$$I_F = \frac{V_{out} - V_{in}}{R_F} \approx \frac{V_{out}}{R_F}$$

Closed-Loop Parameters?

Open-Loop Parameters: $Gain = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$

$$= R_{01} (-g_{m3} R_{02})$$

$$\text{Input Imp.} = \frac{1}{g_{m1}}$$

$$\text{Output Imp.} = R_{02}$$

$$K = -\frac{1}{R_F}$$



$$\text{Closed-Loop Gain} = \frac{-g_{m3} R_{02} R_{01}}{1 + \frac{1}{R_F} (+g_{m3} R_{02} R_{01})}$$

$$\text{--- Input Imp} = \frac{1/g_{m1}}{1 + \frac{g_{m3} R_{02} R_{01}}{R_F}}$$


$$\text{--- Output Imp} = \frac{R_{02}}{1 + \frac{g_{m3} R_{02} R_{01}}{R_F}}$$

Example

A_1

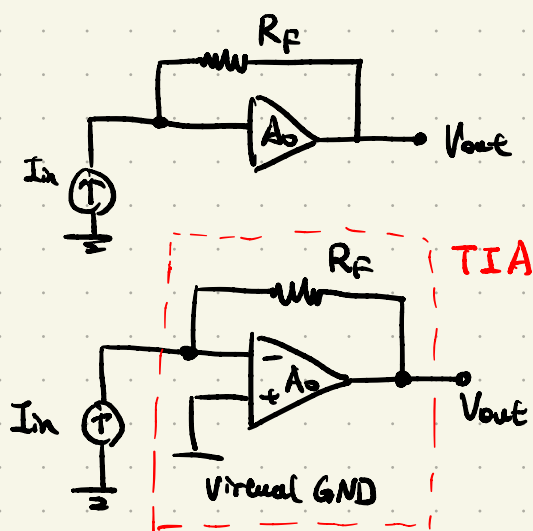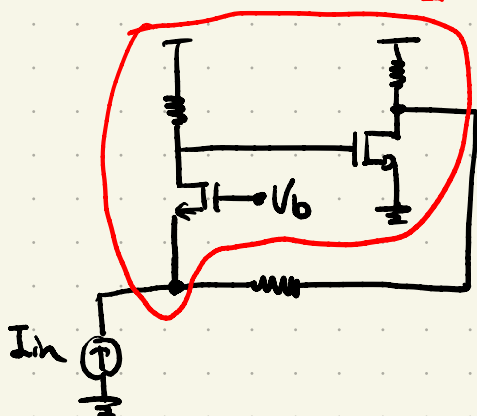


Open-Loop Parameters

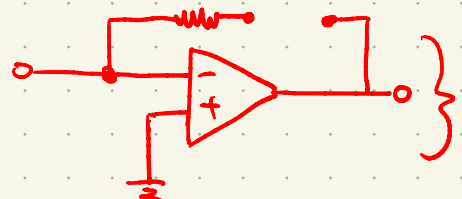

Defer this later.

Closed-Loop Parameters

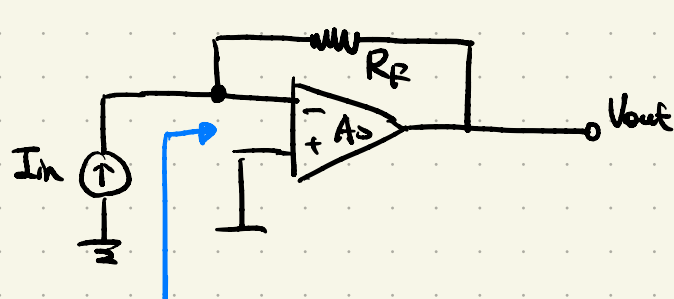


$$\frac{V_{out}}{V_{in}} = -I_{in}$$


$$\Rightarrow \frac{V_{out}}{I_{in}} = -R_F$$

Miller's:
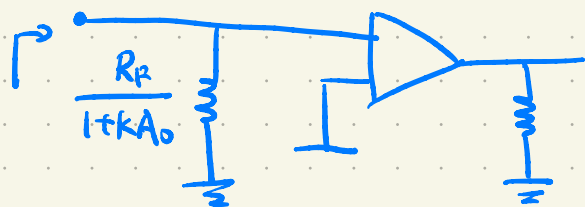
$$\text{Input Imp.} = \frac{R_F}{1+A_0}$$



Q: Find the loop gain of the circuit.

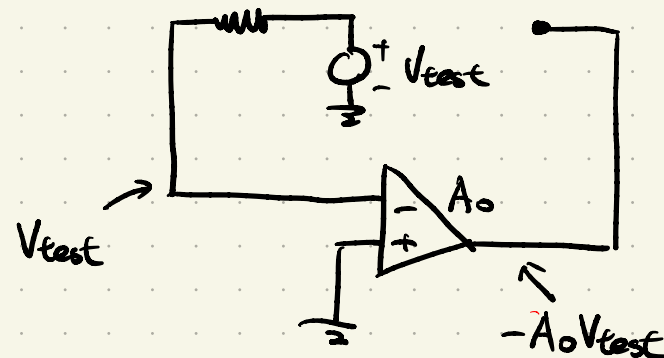


$$\frac{V_F}{V_{test}} = -A_0$$

$$\text{Loop Gain} = A_0$$

Current-Voltage Feedback

Transconductance Amp.

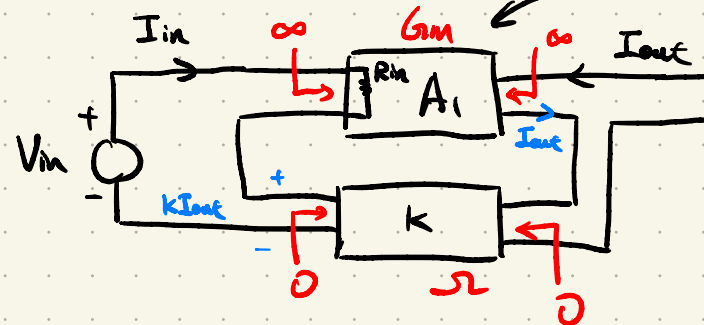

Closed-Loop Gain:

$$(V_{in} - kI_{out}) G_m = I_{out} \Rightarrow \frac{I_{out}}{V_{in}} = \frac{G_m}{1 + kG_m}$$

Closed Loop Input Imp:

$$V_{in} - (I_{in} R_{in}) G_m k = I_{in} R_{in}$$

$$\Rightarrow \frac{V_{in}}{I_{in}} = R_{in} (1 + G_m k)$$