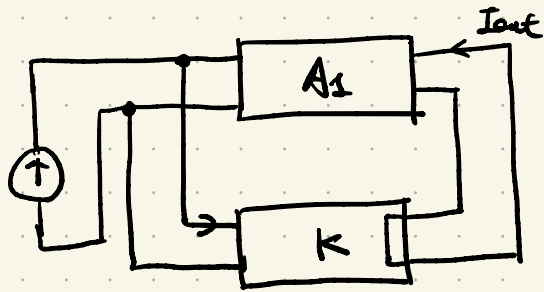


Lec 40

- Current-Current Feedback
- Applications of Feedback in Power Management
- Problems of Loading in feedback Circuits

• Current-Current Feedback




$$\frac{I_{out}}{I_{in}} = \frac{A_1}{1 + KA_1}$$

$$\text{Closed-Loop Input Imp.} = \frac{R_{in}}{1 + KA_1}$$

$$\text{Closed-Loop Output Imp.} = R_{out} (1 + KA_1)$$

Applications of Feedback in Power Management

① Voltage Regulators

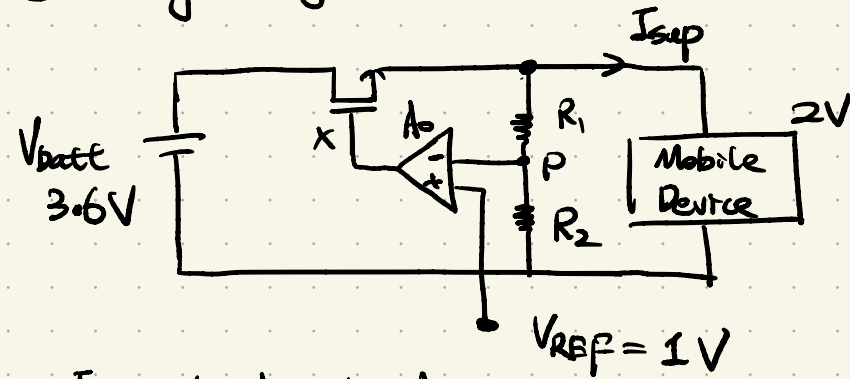

I_{sup} : 10mA – 100mA
(servo loop)


V_{sup} wants to drop
 $\Rightarrow V_x \downarrow \quad V_x \uparrow \quad V_{as} \uparrow$

MOS device can operate in

(a) triode region (as a voltage-controlled resistor)








(b) saturation region (as a source follower)

② Current Regulator


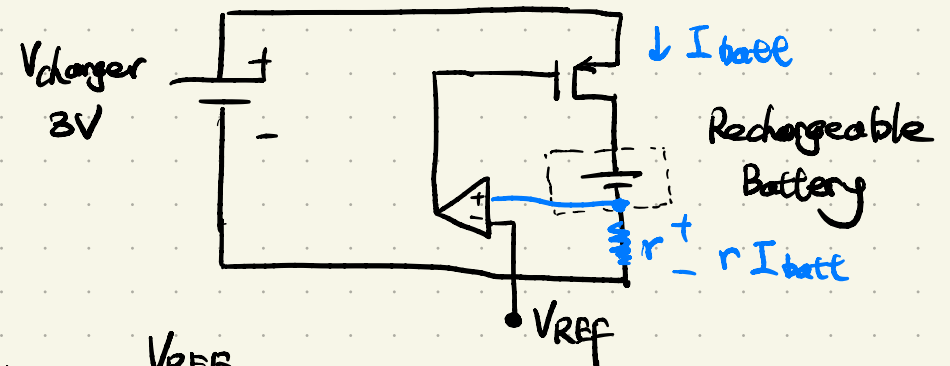


$$I_{batt} = \frac{V_{REF}}{r}$$

Problem of Loading in Feedback Circuits

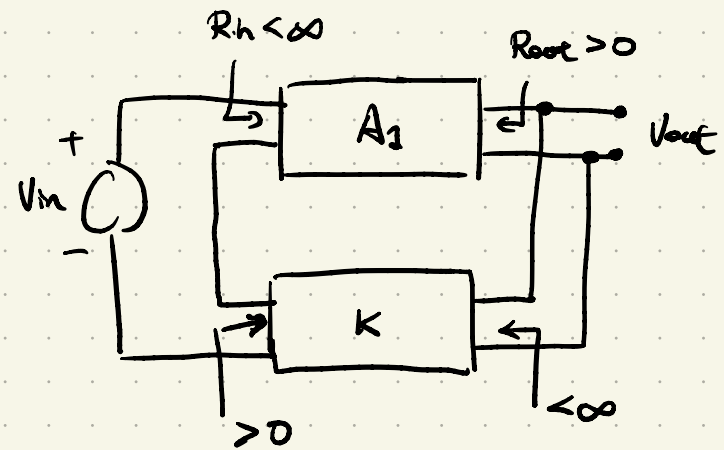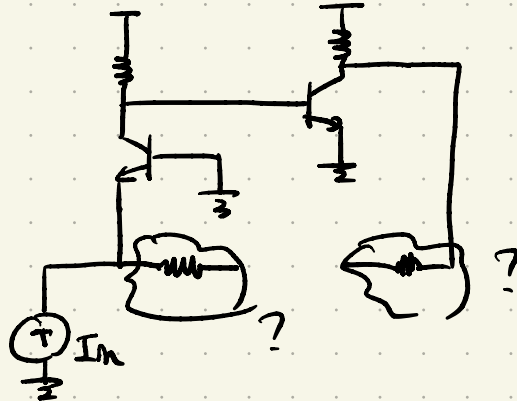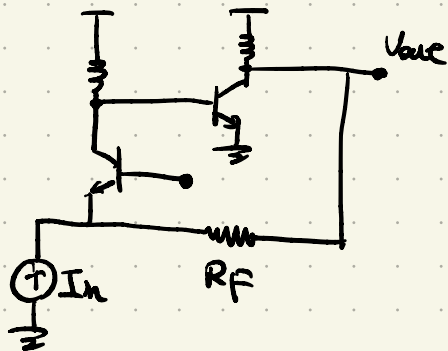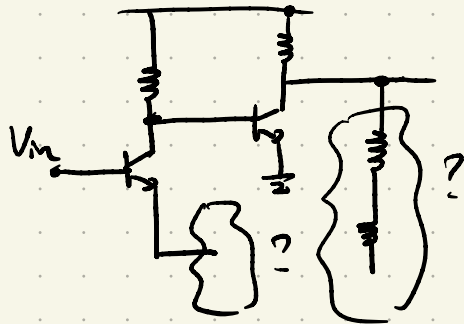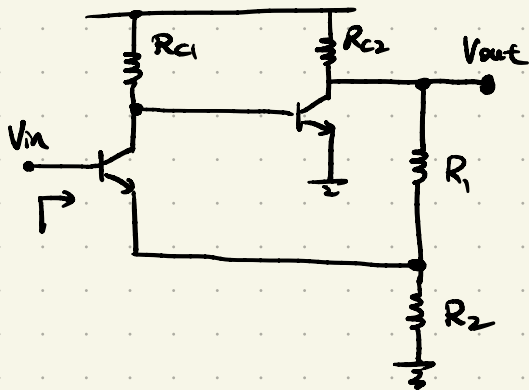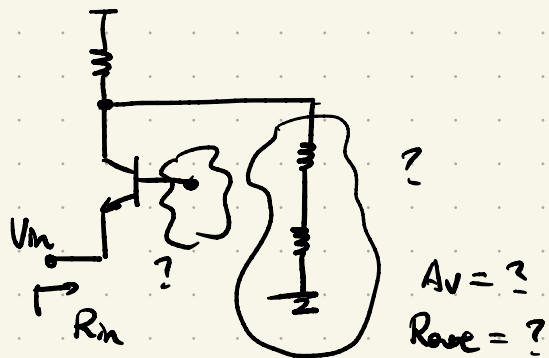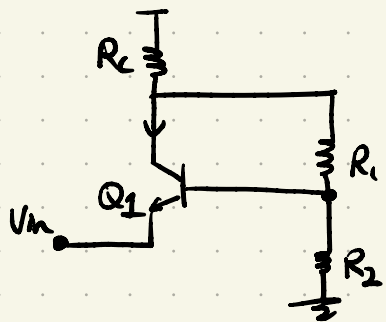

Example

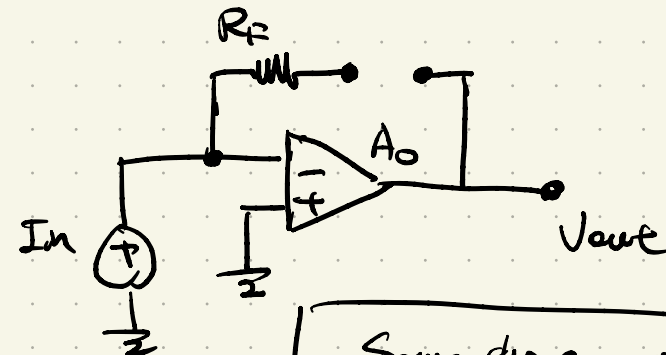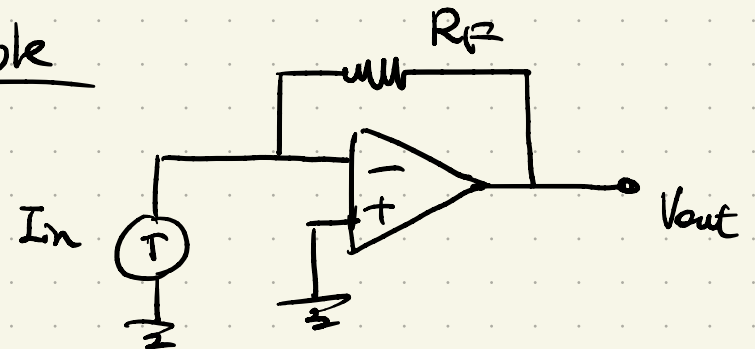

Something will go wrong if we want to find Open-loop parameters.