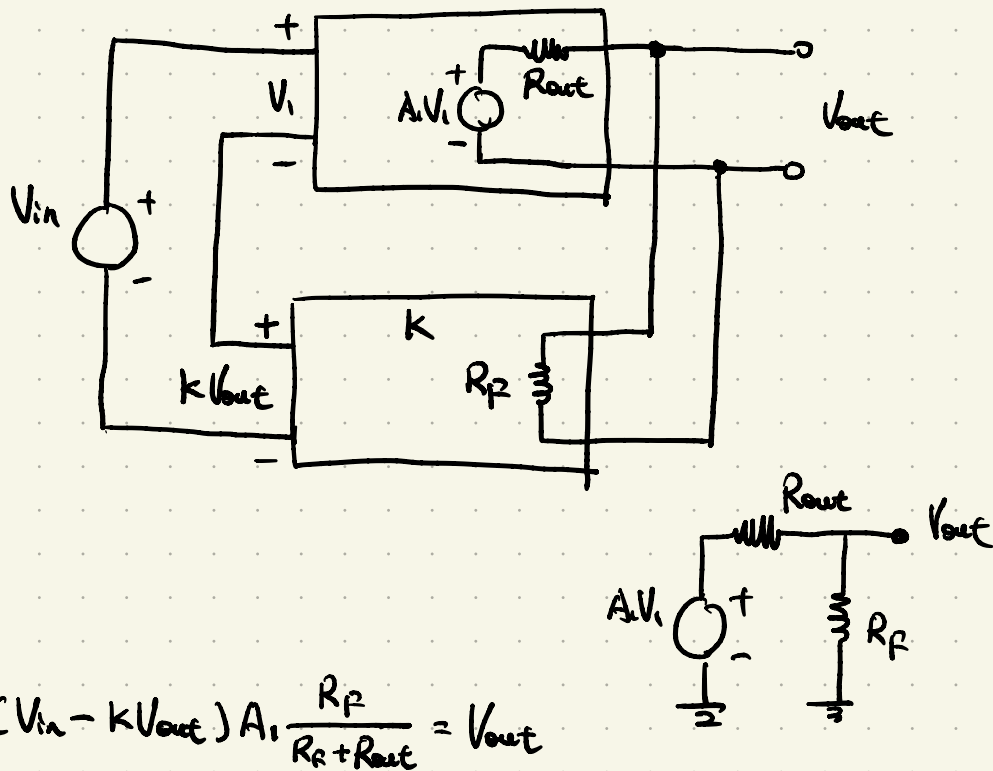


Lec 41



- Accurate Analysis of Feedback Circuits
- Opening the loop properly
- Calculation of Feedback Factor

Illustrative Example



Opening the Loop Properly


Example

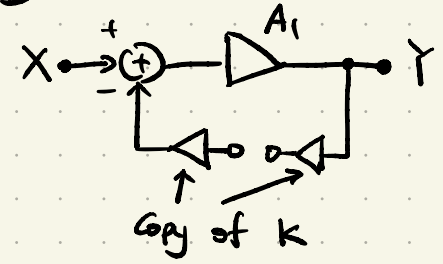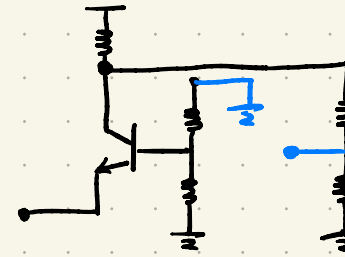


Voltage - Voltage	
Voltage - Current	
Current - Voltage	
Current - Current	

Example

$$V_A = \infty$$

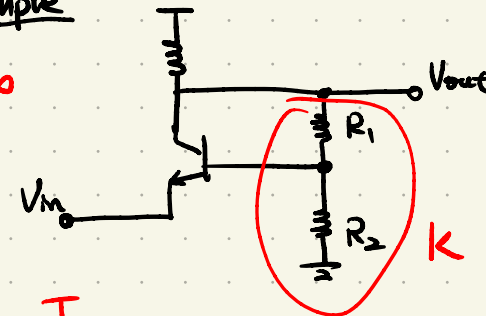



$$R_{out} = R_c \parallel (R_1 + R_2)$$

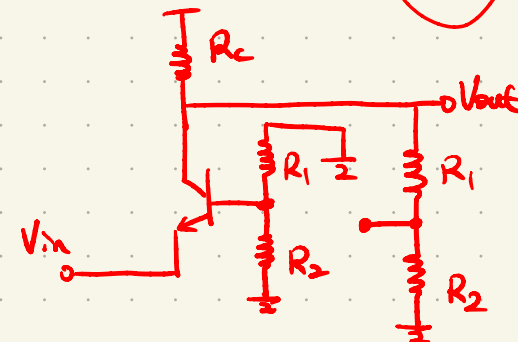

$$A_1 \approx g_m [R_c \parallel (R_1 + R_2)]$$

$$R_{in} = \frac{1}{g_m} + \frac{R_1 \parallel R_2}{1 + \beta}$$

Example

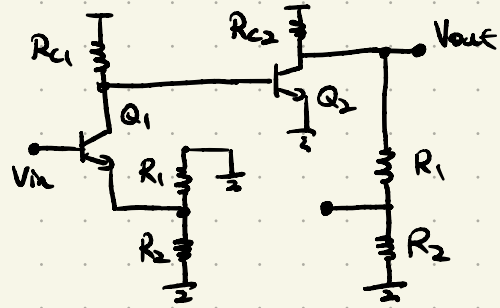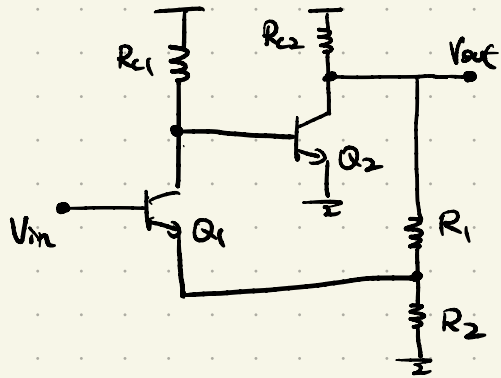


Open-loop Gain:

$$\frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}} = \left\{ -g_{m2} [R_{c2} \parallel (R_1 + R_2)] \right\} \times \frac{-(R_{c1} \parallel R_{a2})}{\frac{1}{g_{m1}} + (R_1 \parallel R_2)}$$

Open-loop Input Imp. = $r_{\pi 1} + (R_1 \parallel R_2)(\beta + 1)$

Open-loop Output Imp. = $R_{c2} \parallel (R_1 + R_2)$

Example

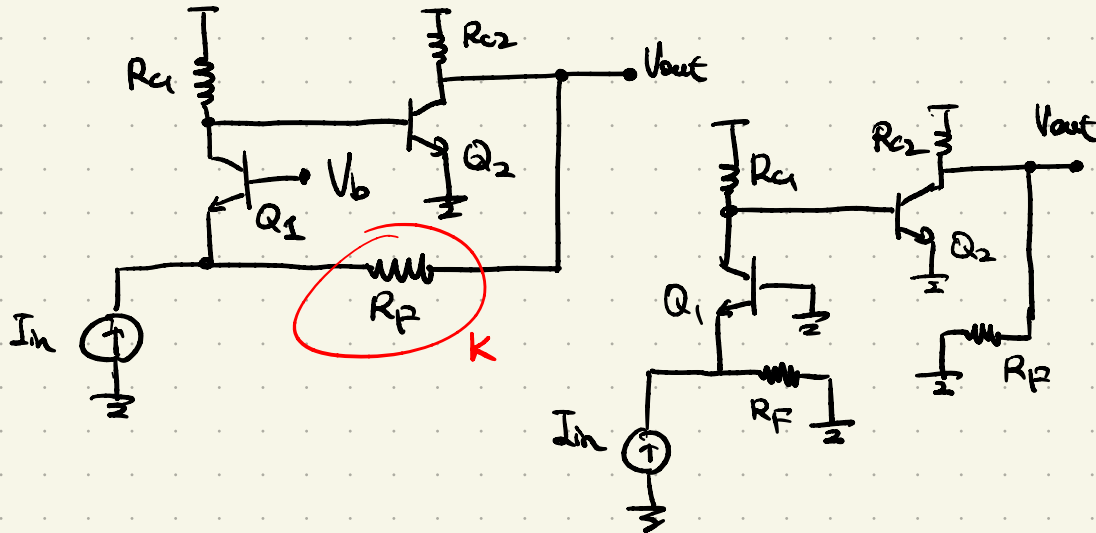

Open-loop Calculations:

$$\text{Gain: } \frac{V_{out}}{I_{in}} = \frac{V_x}{I_{in}} \cdot \frac{V_{out}}{V_x}$$

$$= \left[\frac{I_{in} \cdot R_F}{R_F + \frac{1}{g_m}} \cdot (R_{c1} \parallel R_{a2}) \right] \times -g_{m2} \cdot (R_{c2} \parallel R_F)$$

Input Imp. $R_{in} = \frac{1}{g_{m1}} \parallel R_F$

Output Imp. $R_{out} = R_{c2} \parallel R_F$

Example

