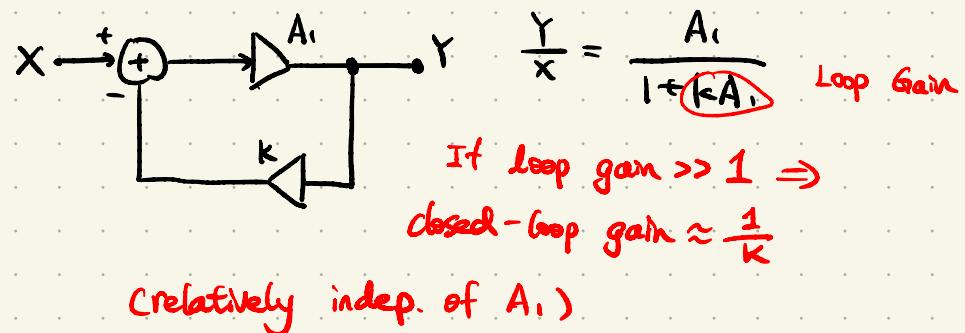


Lec 29

- Application Examples of Feedback
- Summary of feedback concepts
- Properties of Negative Feedback

Review of Lec 28




• Summary of Feedback Concepts


① We sacrifice the open-loop gain to benefit from negative feedback.

② The feedback signal is a good copy of the input signal.

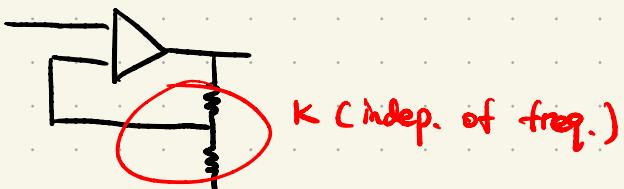③ $Y = \frac{V}{K}$ is a good copy of X but with a scaling factor. e.g. if $K=0.1$ $Y=10\text{ V}$




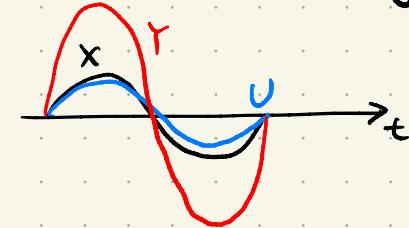⇒ The loop wants to make Y a good copy of X




④ If $kA_1 \gg 1 \Rightarrow$ factors that cause A_1 to vary have less effect on the closed-loop gain

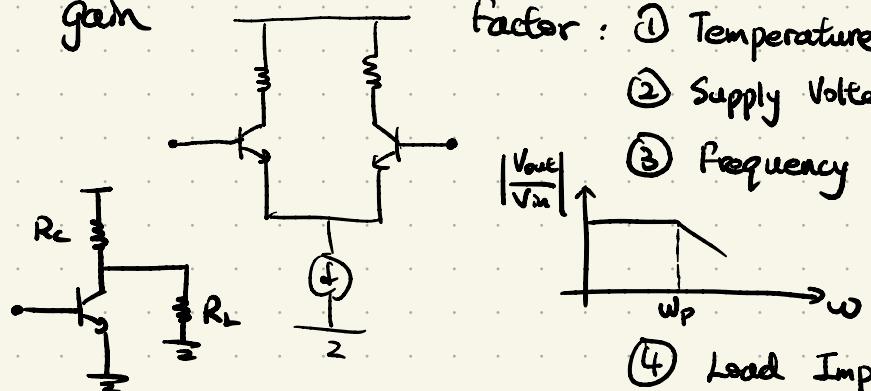- factor : ① Temperature
② Supply Voltage
③ Frequency




④ Load Imp.

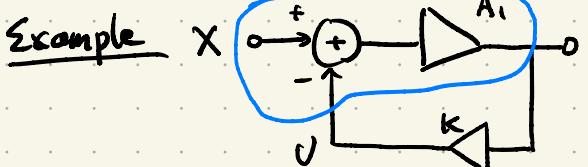


$$I_D = \frac{1}{2} \ln \left(\frac{W}{L} C (V_{in2} - V_{in1} - V_{TH})^2 \right)$$

For small signal operation:
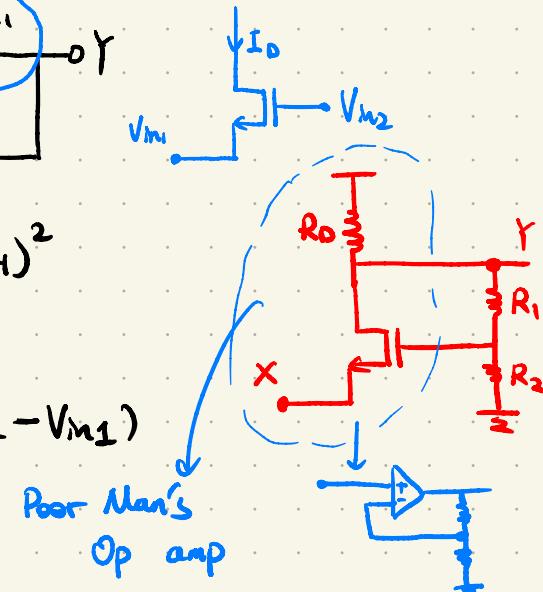
$$I_D = g_m V_{as} = g_m (V_{in2} - V_{in1})$$



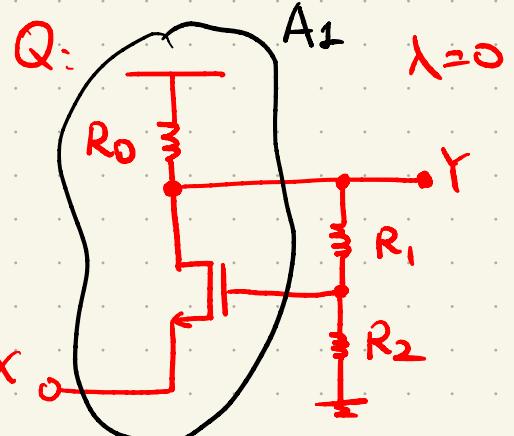

$$\frac{Y}{X} = ? \quad R_1 + R_2 \text{ is very large}$$


$$= \frac{A_1}{1+KA_1} \quad A_1 = g_m R_D$$

$$K = \frac{Y}{X} = \frac{R_2}{R_1 + R_2}$$

$$\frac{Y}{X} = \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$

Loop Gain: $g_m V_{test}$
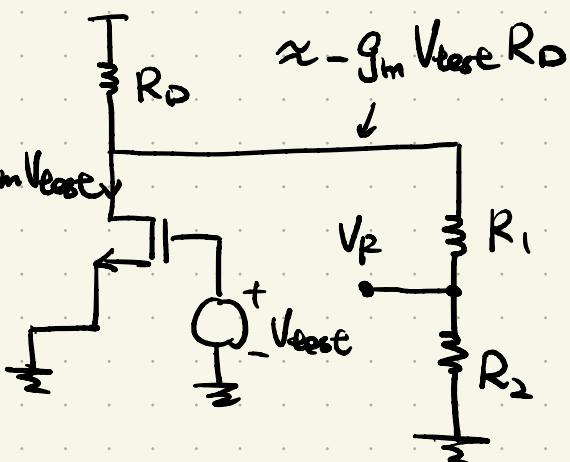
$$= -\frac{V_F}{V_{test}} = \frac{g_m R_D R_2}{R_1 + R_2}$$



$$V_F = -g_m V_{test} R_D \frac{R_2}{R_1 + R_2}$$

Properties of Negative Feedback

$$\frac{Y}{X} = \frac{A_1}{1+KA_1} \approx \frac{1}{K} \quad \text{if } KA_1 \gg 1$$

① Gain Desensitization: $\frac{Y}{X}$ is less sensitive to temp. supply. --- than A_1 is

② Bandwidth Extension: Greater BW for the closed loop system

③ Modification of Input and Output Impedances

④ Higher Linearity

