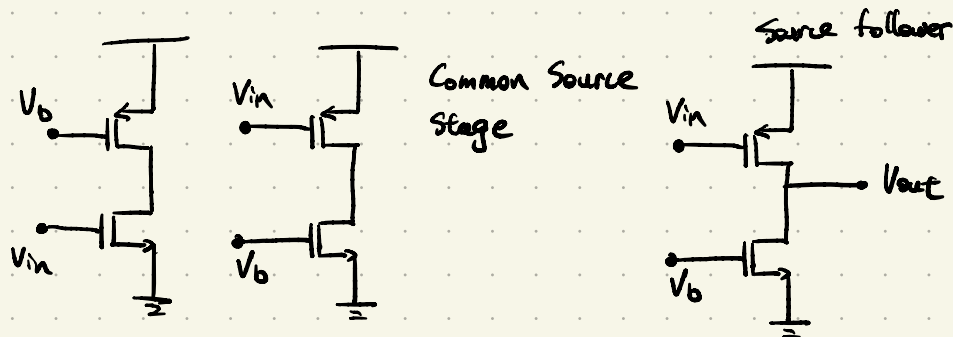



## Lec 5: Problem of Biasing; Intro to Current Mirrors

- The Need for Current Sources
- Problem of Biasing Current Sources
- Current Mirrors


- Current Sources are everywhere:



- Problem of Biasing Current Sources

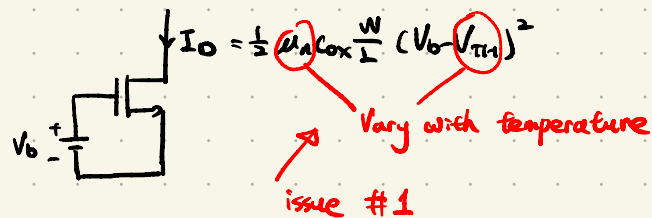


How to generate  $V_b$ :

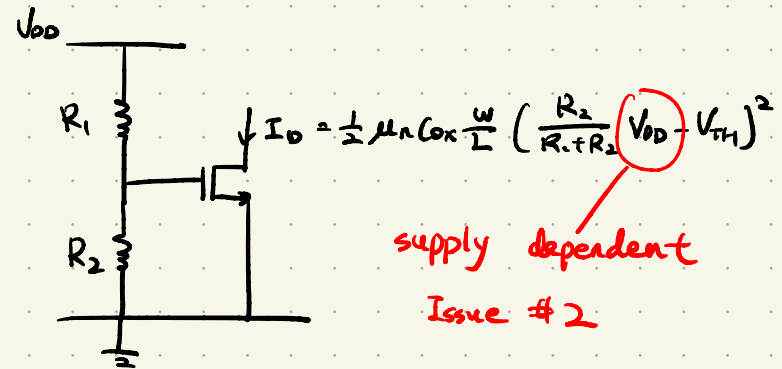


- Current Mirror  
Basic Concept

First, build one "golden" current source using a bandgap circuit.

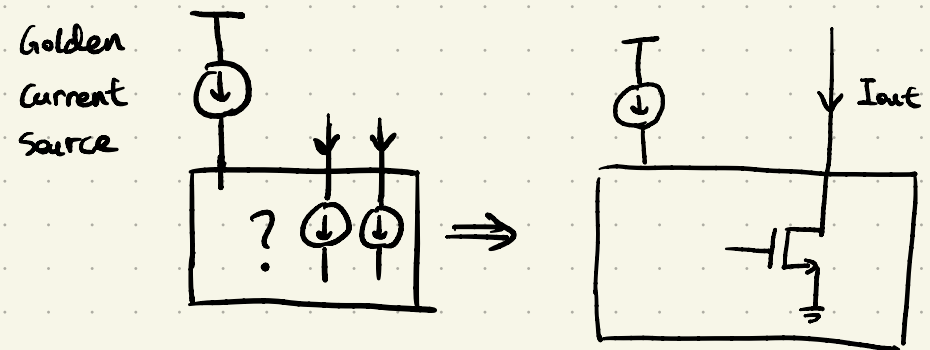Next, we clone this current source to build many others





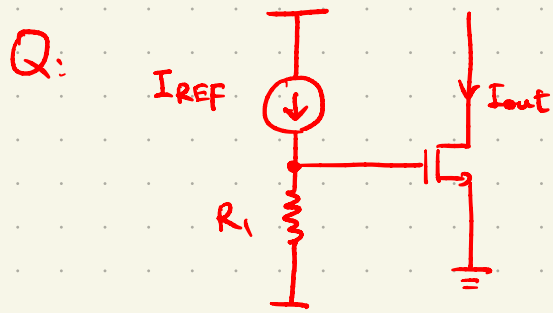

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (R_1 I_{REF} - V_{TH})^2$$

Vary with temperature



## Observations

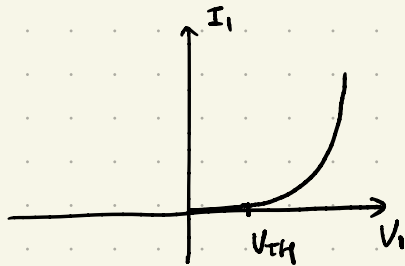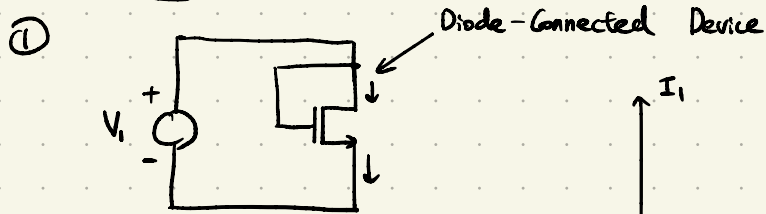

If  $M_1$  is on, it is in sat.


$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_i - V_{TH})^2 \quad V_i \geq V_{TH}$$

②

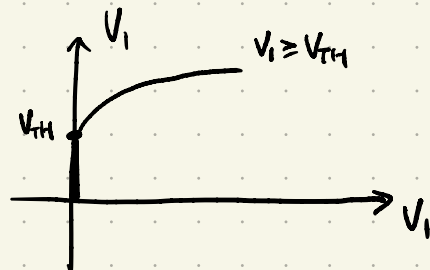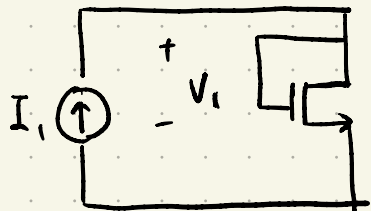


$$V_i = \sqrt{\frac{2I_1}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

③

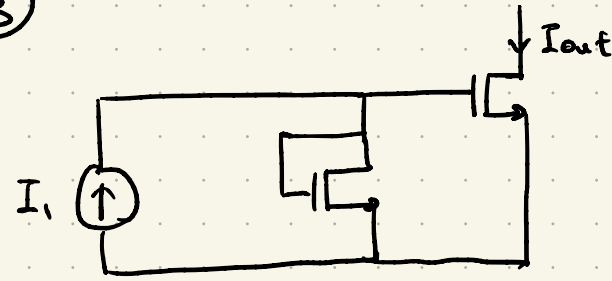


$$\begin{aligned} I_{out} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_i - V_{TH})^2 \\ &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 \left[ \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{TH} - V_{TH} \right]^2 \\ &= \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \cdot I_1 \end{aligned}$$

## Current Mirror

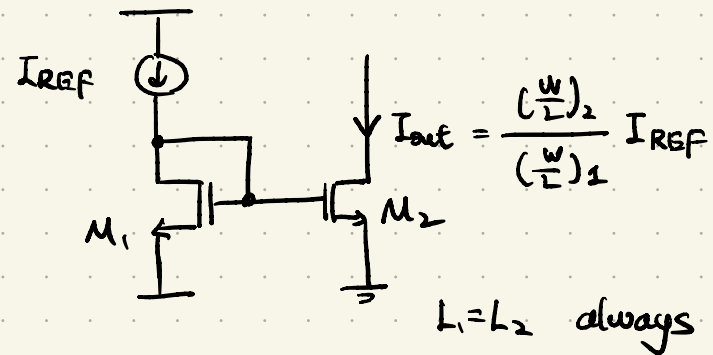

Select  $\frac{W_2}{W_1}$  accordingly

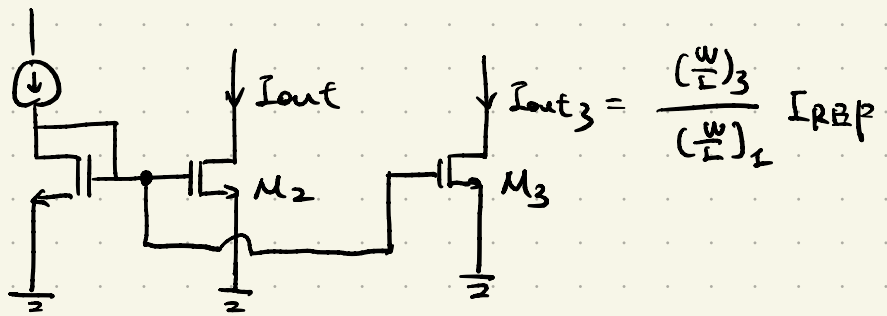

$$I_{out3} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} I_{RBP}$$