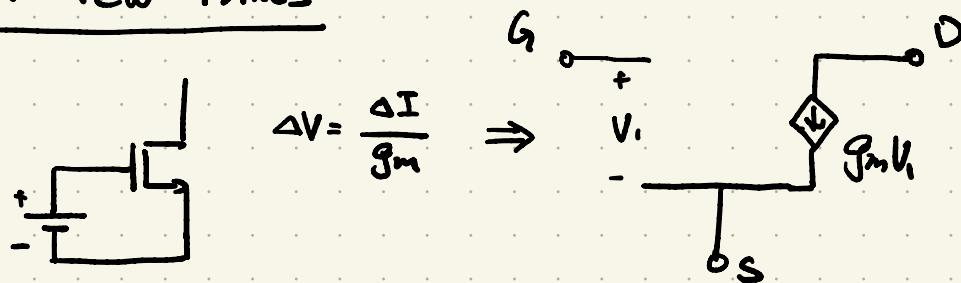


# Lec 14

- Applications of some Circuit Techniques
- Small-Signal Analysis of MOS Diff. Pair.

## A Few Points

①



②

$$V_x - V_y = -R_D \sqrt{2\mu_n C_o x \frac{W}{L}} I_{ss} (V_{m1} - V_{m2})$$

$$= -R_D \sqrt{2\mu_n C_o x \frac{W}{L}} I_{ss} (2\Delta V)$$

$$V_x - V_y = -R_D (I_{D1} - I_{D2})$$

$$I_{D1} - I_{D2} = \sqrt{2\mu_n C_o x \frac{W}{L}} I_{ss} (2\Delta V)$$

$$I_{D1} + I_{D2} = I_{ss}$$

$$\Rightarrow I_{D1} = \frac{I_{ss}}{2} + \sqrt{2\mu_n C_o x \frac{W}{L}} \Delta V$$




change in  $I_{D1}$

$$V_{as1} \text{ changes by } \frac{\sqrt{2\mu_n C_o x \frac{W}{L}} I_{ss}}{g_m} \Delta V = \Delta V$$

$$g_m = \sqrt{2\mu_n C_o x \frac{W}{L}} I_0$$

$\Rightarrow V_p$  doesn't change  $\Rightarrow P$  is ac GND


## Small-Signal Operation

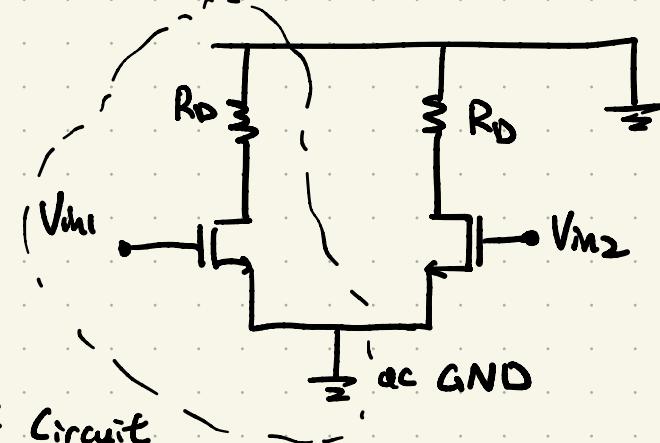


Half Circuit

$$\frac{V_x}{V_{m1}} = -g_m R_D \Rightarrow \frac{V_x - V_y}{V_{m1} - V_{m2}} = -g_m R_D$$


## Example

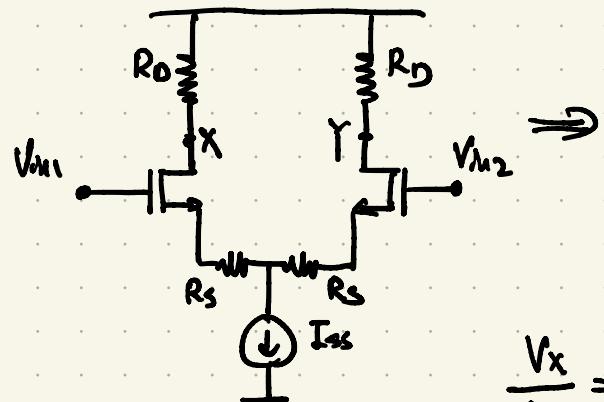
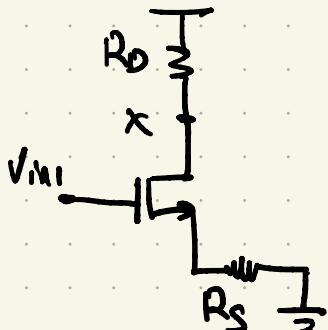
$$\frac{V_x}{V_{m1}} = - \frac{R_0}{\frac{1}{g_m} + R_S}$$




## Example

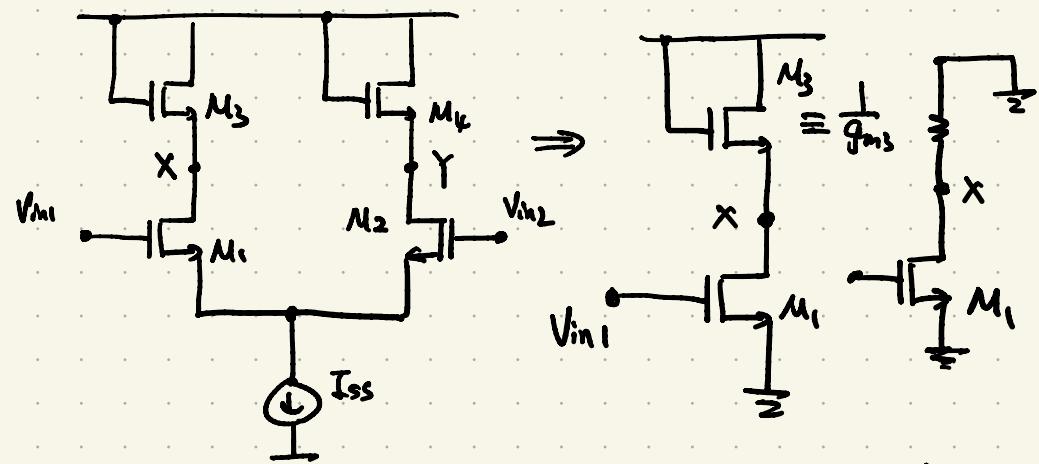

$$A_v = -g_{m1} \frac{1}{g_{m3}}$$

## Example

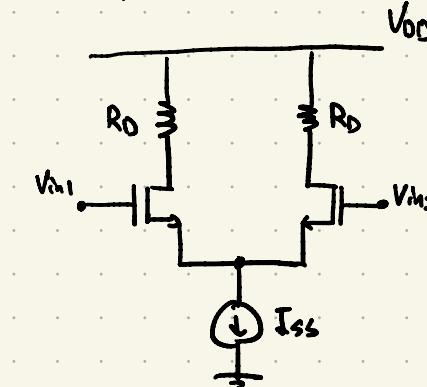

$$W \rightarrow 2W$$

what happens to  $A_v$ ?

$$A_v = -g_m R_D$$

$$g_m = \sqrt{2 \mu_n C_o \frac{W}{L} I_D}$$

$$g_m \rightarrow \sqrt{2} g_m$$

$$A_v \rightarrow \sqrt{2} A_v$$

## Example

What happens if both  $W$  and  $I_D$  are doubled?

$$g_m \rightarrow 2g_m \Rightarrow A_v \rightarrow 2A_v$$


## Example

What happens if the temperature rises?


$$\mu_n \downarrow g_m \downarrow \Rightarrow A_v \downarrow$$

## P-Type Diff. Pair



P

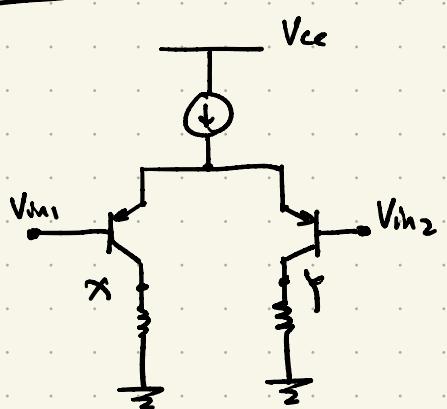

N

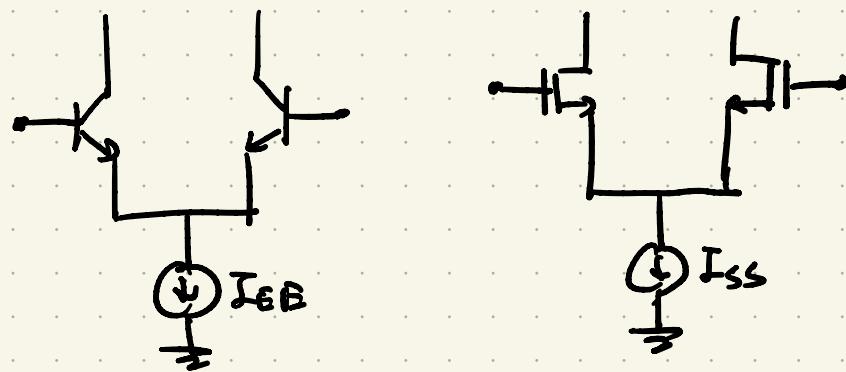


## Example

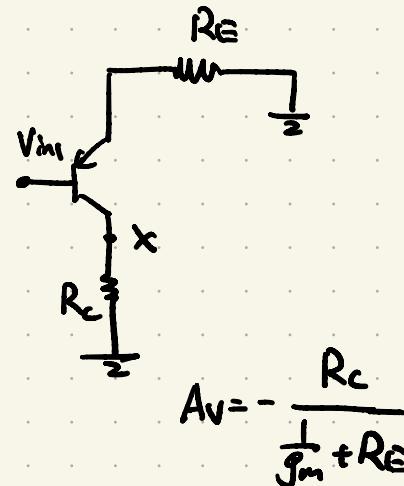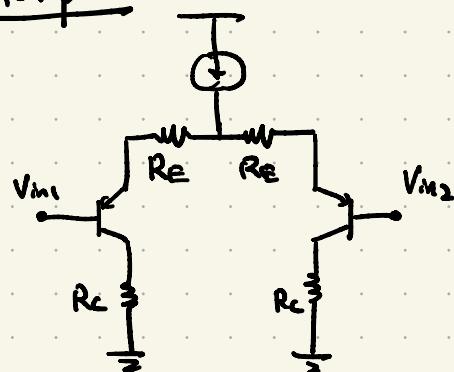


$$A_v = -\frac{R_c}{\frac{1}{g_m} + R_E}$$

## Example

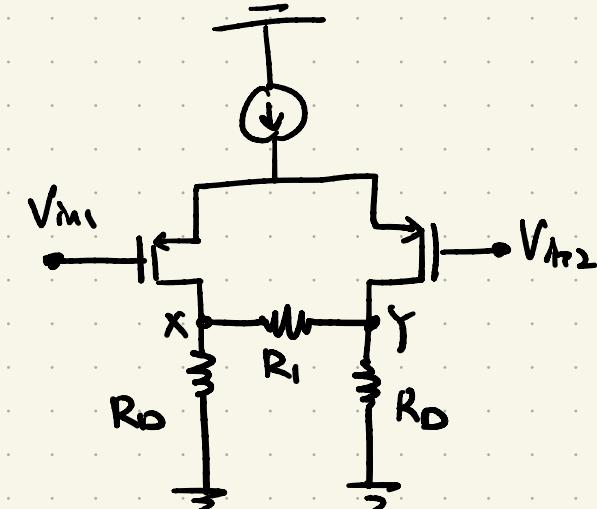
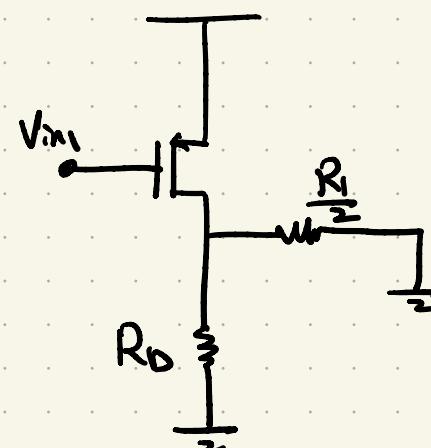
$$\frac{R_1}{2}, \frac{R_2}{2}, \frac{R_r}{2}$$



$$A_v = -g_m \left( R_D // \frac{R_l}{2} \right)$$