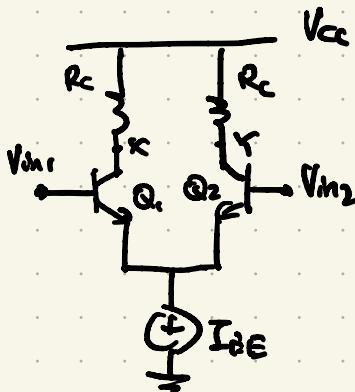


Lec 11

- Additional Examples on Bipolar Diff. Pair
- Intro. to MOS Diff. Pair



Example

$$I_{BEE} = 1 \text{ mA} \quad R_c = 1 \text{ k}\Omega$$

$$I_S = 2 \times 10^{-18} \text{ A} \quad I_c = I_S \exp \frac{V_{BE}}{V_T}$$

- Determine the bias conditions of Q₁ and Q₂.
- Construct the input-output charac.
- Voltage gain.


$$V_{BE} = V_T \ln \frac{I_c}{I_S}$$

Bias conditions:

$$I_{c1} = I_{c2} = \frac{I_{BEE}}{2}$$

$$V_{BE1} = V_{BE2} = 862 \text{ mV}$$

(b) $R_c I_{BEE} = 1 \text{ V}$

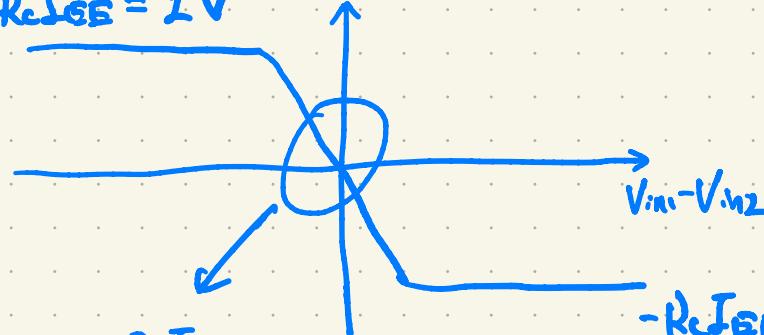


$$\text{Slope} = -\frac{R_c I_{BEE}}{2V_T} = -19.2$$

$$\begin{aligned} \text{Small-Signal Gain} &= -g_m R_c \\ &= -19.2 \end{aligned}$$

Example

$$R_1 = R_2 = R$$

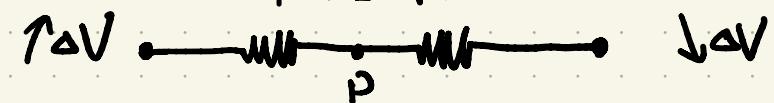

what happens to P ?


$$\text{Current} = \frac{2\Delta V}{2R} = \frac{\Delta V}{R}$$

Voltage drop across R₁:


$$\frac{\Delta V}{R} \cdot R = \Delta V$$

⇒ V_p is constant

Example

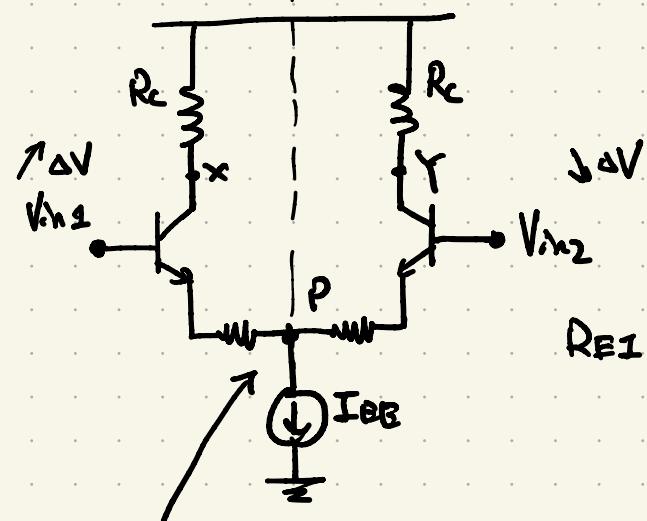

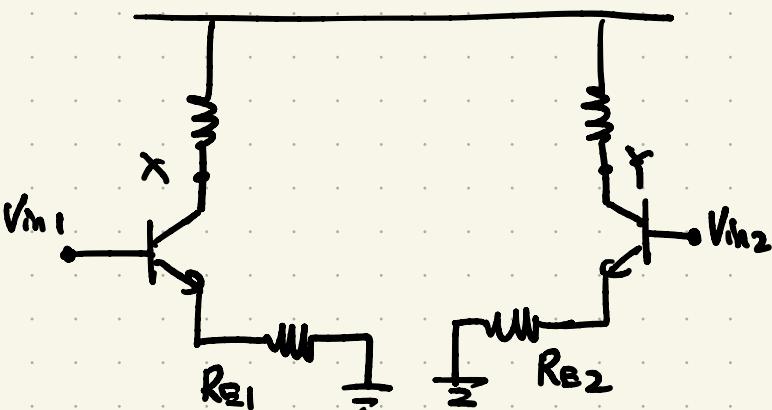
V_P does not change with time
 $\Rightarrow P$ is ac GND



$$\frac{V_x}{V_{x_{in1}}} = - \frac{R_C}{\frac{1}{g_m} + R_{E1}}$$


$$\Rightarrow \text{Diff. Gain} = - \frac{R_C}{\frac{1}{g_m} + R_E}$$

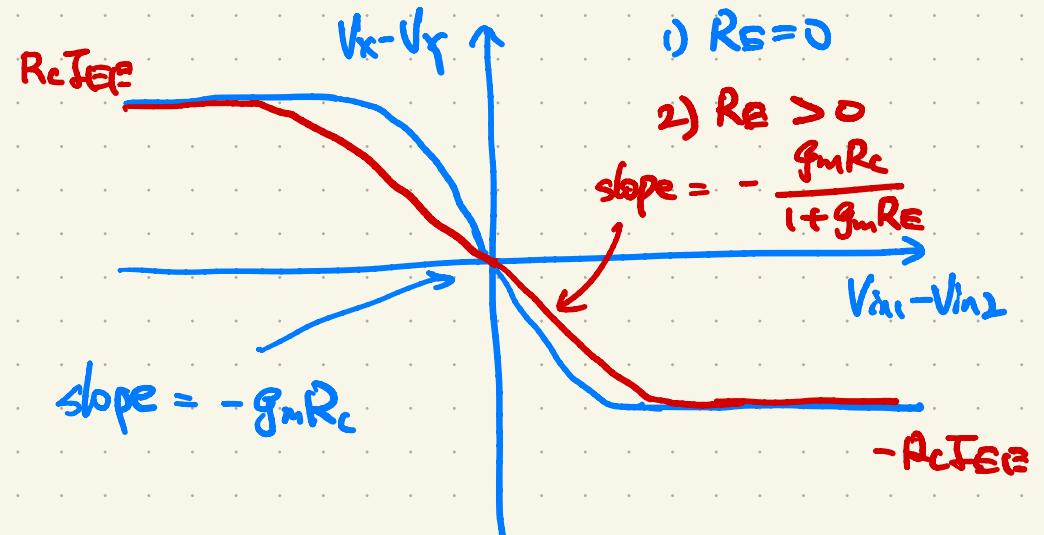Quiz : Construct the input-output charac. of the degen. diff. pair




Emitter degeneration improves the linearity

Example

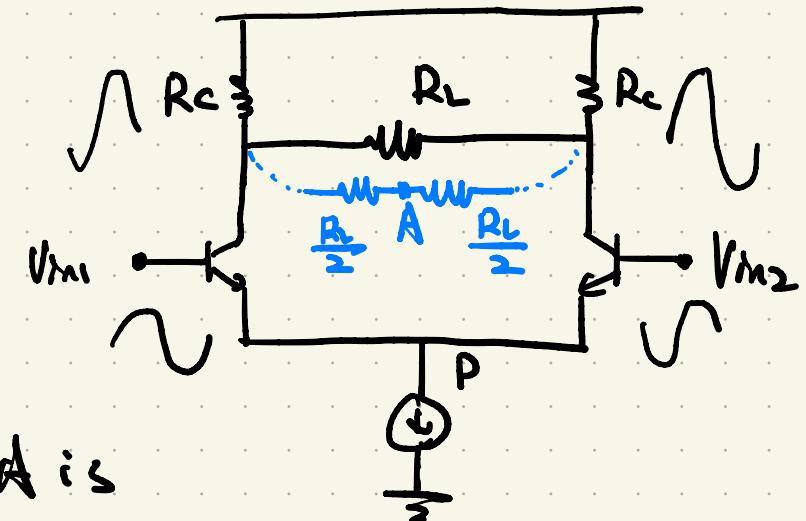


Node A is
ac GND

Half - Circuit Equivalent

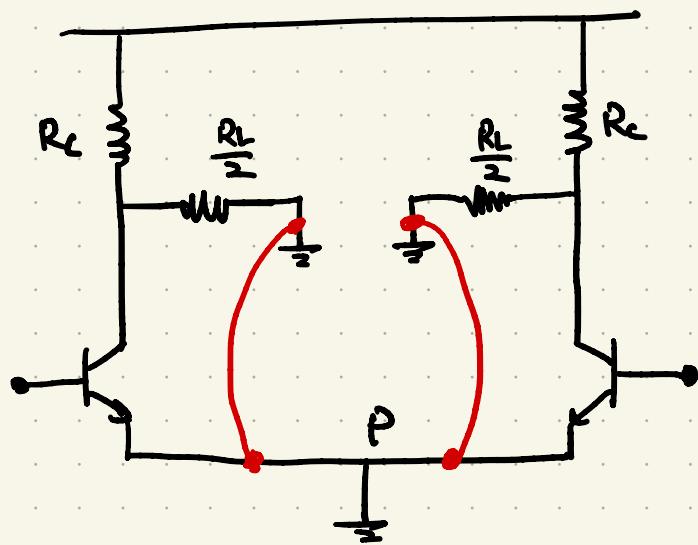

$$A_v = -g_m \left(R_C / \frac{R_L}{2} \right)$$

Example

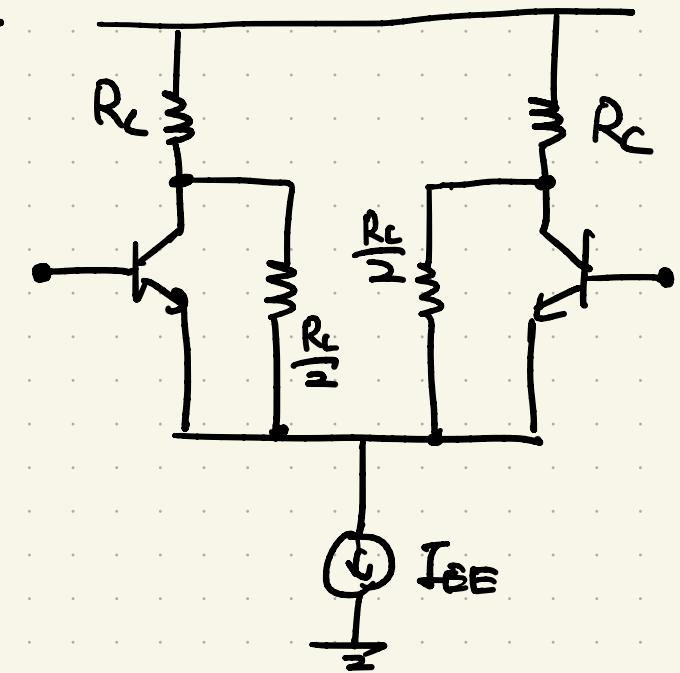

Example

$$V_A < \infty$$

$$A_v = -g_m (R_C / r_o)$$

