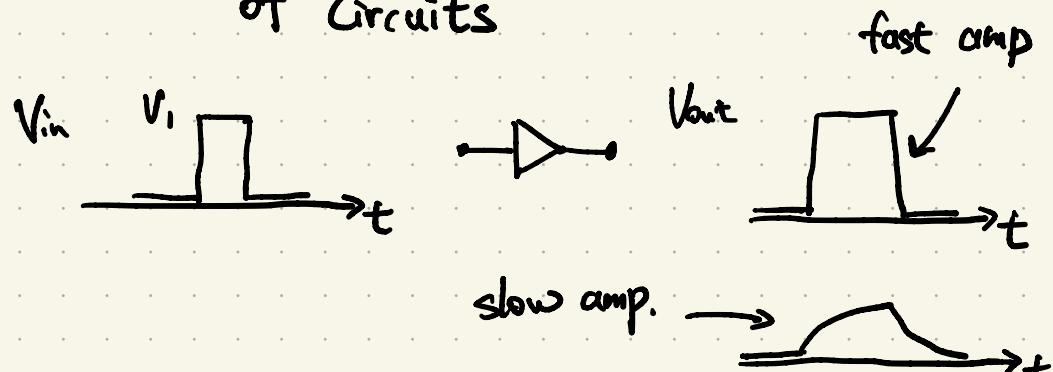


Lec 17 Frequency Response

- Objective & Motivation
- Circuit Theory Concepts

Objective: Determine the speed limitation of Circuits



Why?


High speed circuits are everywhere:

Wi-Fi: 2.4 GHz, 5 GHz Bluetooth: 2.4 GHz

GPS: 1.5 GHz, automotive radars: 26 GHz


Microprocessors: 4-5 GHz

Example

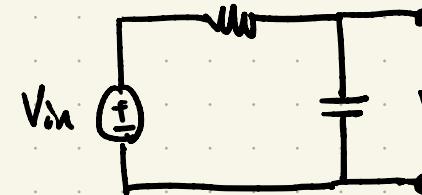

$$V_{out} = V_i (1 - e^{-\frac{t}{RC}})$$

$$I = R, C$$

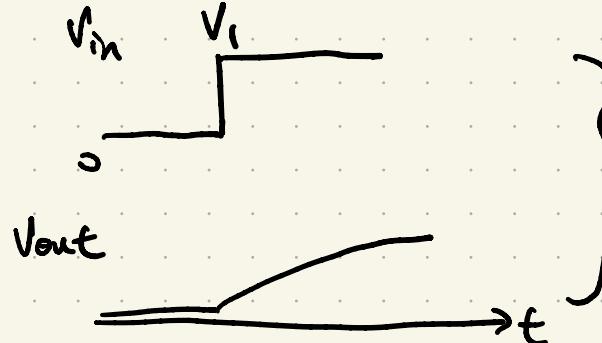


(a) Time-Domain Analysis's

To improve the speed, we must minimize R, C



(b) Frequency-Domain Analysis's

Formulates the response to sinusoidal

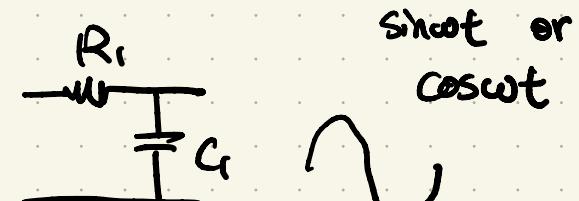

- ①
- ②
- ③

Need for Frequency Response

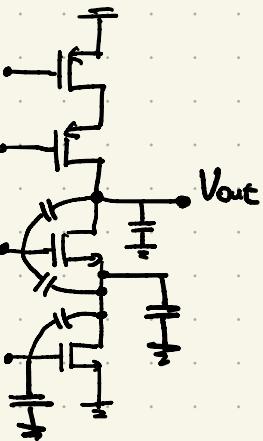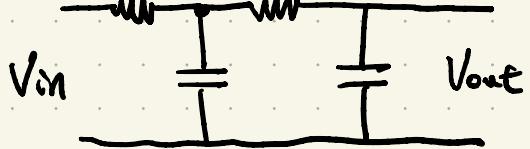

Circuit Theory Concepts

① Time Domain Freq. Domain

$$V_i \quad I_i \quad C_i \quad I_i = C_i \frac{dV_i}{dt}$$

$$I_i = C_i S \cdot V_i \Rightarrow \frac{V_i}{I_i} = \frac{1}{C_i S}$$

"Impedance"

②

$$V_i = R_i I_i + \frac{1}{C_i} \int I_i dt$$

$$V_i = R_i I_i + \frac{I_i}{C_i S}$$

③

$$V_{out} = \frac{1}{C_i S + R_1} V_{in}$$

Transfer Function

$$= \frac{1}{1 + S C_i R_1} V_{in}$$

$$R_i C_i \frac{dV_{out}}{dt} + V_{out} = V_{in}$$


④ s is generally a complex frequency. But we can assume $S=j\omega$ if the signals of interest are sinusoids.

e.g. $H(s) = \frac{1}{1 + R_i C_i s}$ if V_{in} is a sinusoid, $S=j\omega \Rightarrow H(j\omega) = \frac{1}{R_i C_i j\omega + 1}$


⑤ a complex number $a+jb$ can be represented in the polar form:

$$\text{Magnitude} = \sqrt{a^2 + b^2}$$

$$\text{phase} = \tan^{-1} \frac{b}{a}$$

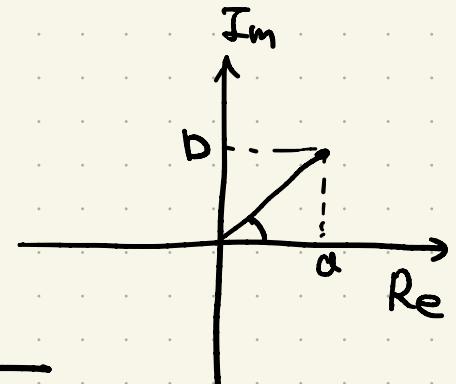


$$|H(j\omega)| = \frac{1}{\sqrt{R_i^2 C_i^2 \omega^2 + 1}}$$

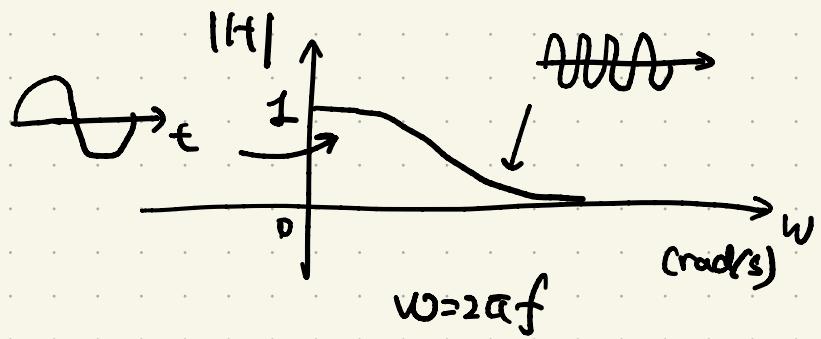


How to compute the freq. response?

- ① Determine the transfer function, $H(s)$
- ② Replace s with $j\omega \Rightarrow H(j\omega)$
- ③ Compute $|H(j\omega)| = \text{Freq. Resp.}$

Example

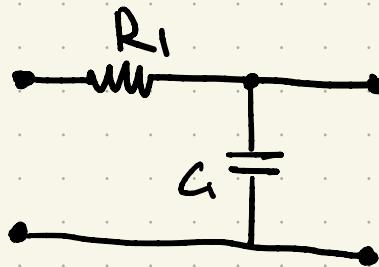
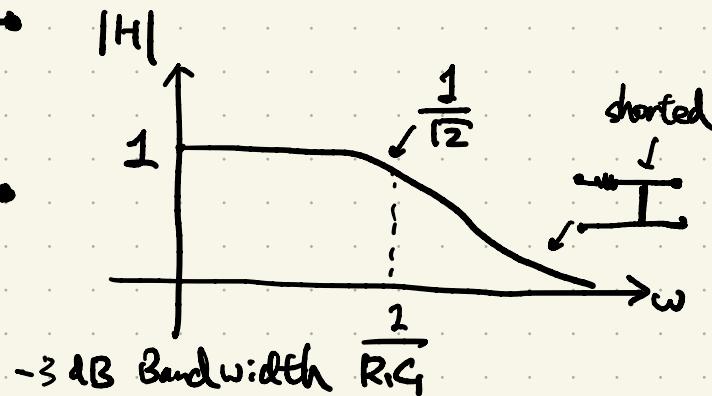
$$H(j\omega) = \frac{1}{\sqrt{1 + \omega^2 R_1^2 C_1^2}}$$



$\frac{1}{\sqrt{2}}$

shorted

$\frac{1}{2}$

dB

-3 dB Bandwidth $\frac{1}{R_1 C_1}$