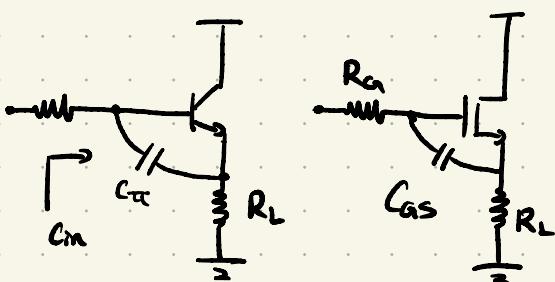


Lec 25

- Output Impedance of Followers
- Freq. Response of Cascades
- Freq. Response of Diff. Pairs
- The Transit Frequency, f_T

Review of Lec. 24




① Input Cap =

$$\frac{C_{pi}}{1 + g_m R_L}, \quad \frac{C_{gs}}{1 + g_m R_L}$$

② Output Impedance of Source Follower
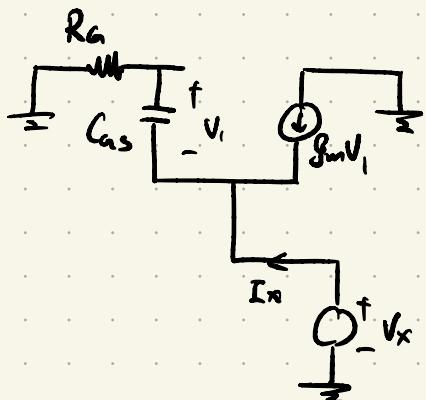
$$\frac{V_x}{I_x} = Z_{out} = \frac{1 + R_L C_{gs} \cdot s}{C_{gs} s + g_m}$$




$$\omega_2 = -\frac{1}{R_L C_{gs}}$$

$$\omega_p = -\frac{g_m}{C_{gs}}$$

• Let's plot $|Z_{out}|$


Case I:

$$g_m < \frac{1}{R_L}$$

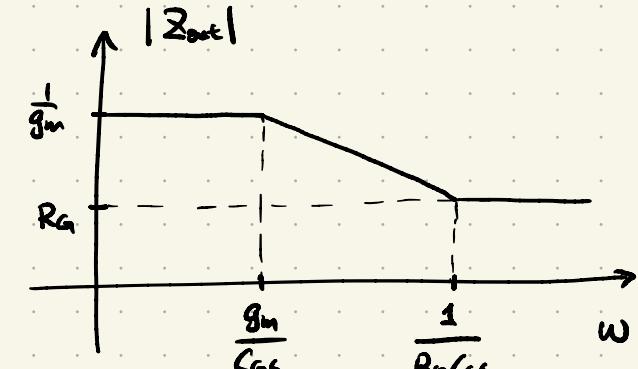



Case II:

$$g_m > \frac{1}{R_L}$$

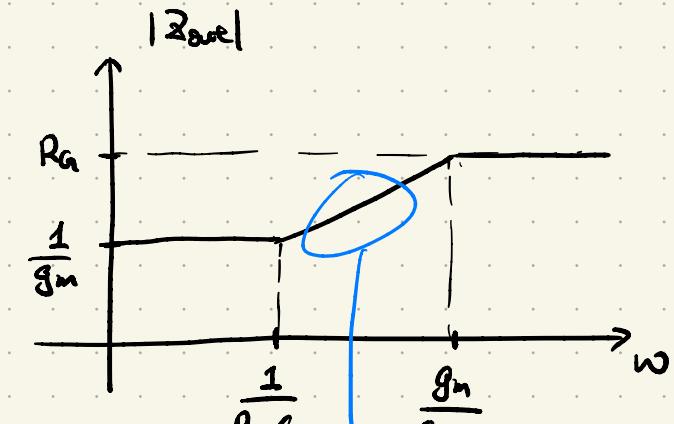

inductive behavior

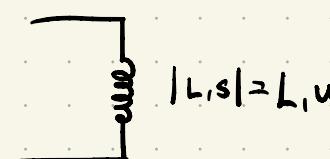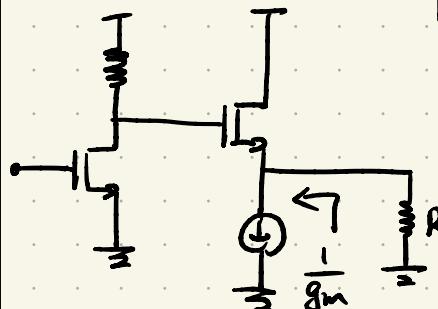
We are interested in the case $\frac{1}{g_m} \ll R_L$ (Case II)



(We can build
"active inductor")

- Freq. Response of Cascades

① Bipolar

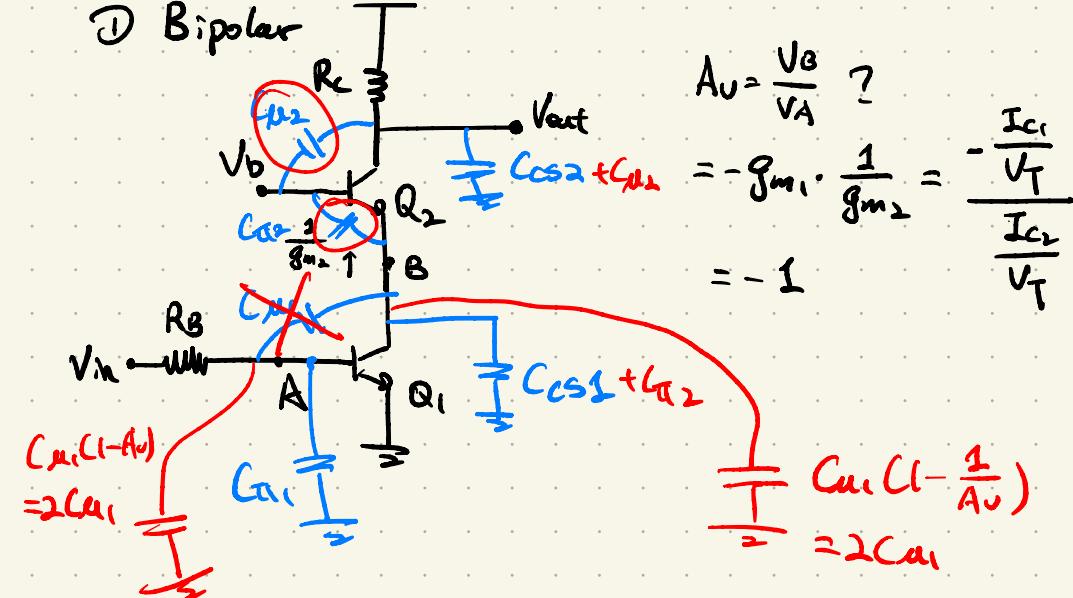


$$W_{P,A} = \frac{1}{(R_B H_r \alpha) (C_{A1} + 2C_{A1})}$$

$$W_{P,out} = \frac{1}{R_C (C_{CS2} + C_{A2})}$$

$$W_{P,B} = \frac{1}{\frac{1}{g_{m2}} (C_{CS1} + C_{A2} + 2C_{A1})}$$

← typically very high

Compare with simple CB stage

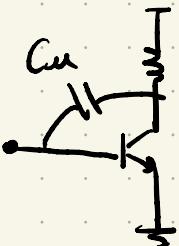


$$C_m = C_{A1}(1 + g_m R_C)$$


(to ground)

has a greater Miller multiplication than cascade structure

- Freq. Response of Diff. Pairs


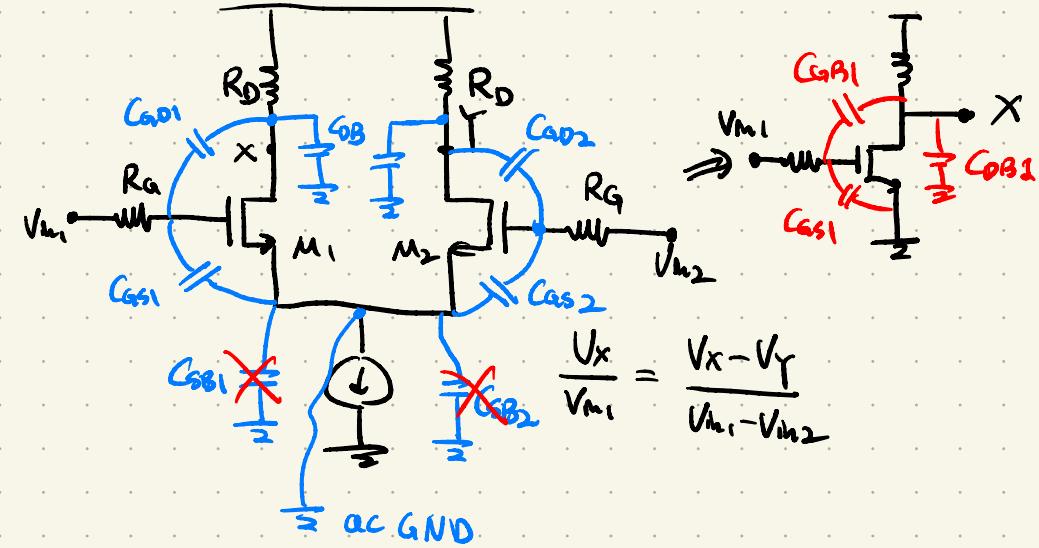


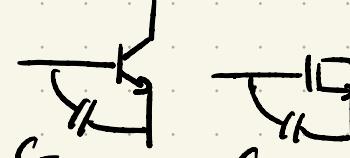The Transit freq., f_T : the freq. at which the current gain of the device drop to 1



$$\left| \frac{I_{out}}{I_m} \right| CS=j\omega_T = 1$$

$$\left| \frac{I_{out}}{I_m} \right| \omega_T = 2\pi f_T$$

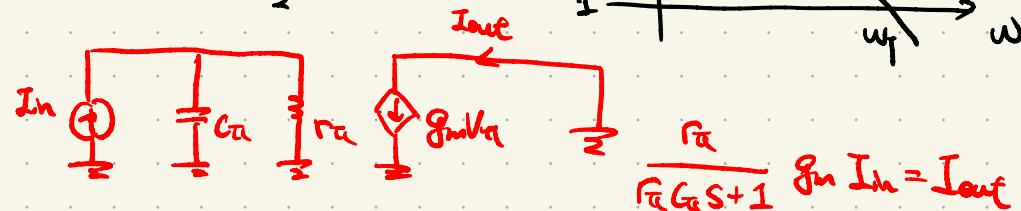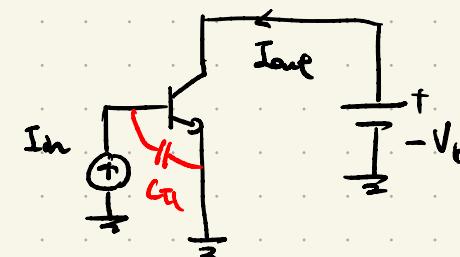

$$\frac{I_m}{R_C g_m + 1} g_m I_m = I_{out}$$

$$\frac{I_{out}}{I_{in}} = \frac{\cancel{g_m} \cancel{r_o} \beta}{r_o C_{in} s + 1} \quad | \frac{I_{out}}{I_{in}} (s - j\omega) |^2 = \frac{\beta^2}{C_{in}^2 C_{out}^2 \omega^2 + 1} = 1$$

$$\Rightarrow w_T = \frac{\beta}{r_o C_{in}} = \frac{g_m}{C_{in}}$$

MOS: $w_T = \frac{g_m}{C_{GS}}$

$$f_T = \frac{g_m}{2\pi C_{GS}}$$

For integrated circuits:

$f_T \approx$ several hundred GHz

Example:

How to maximize f_T ?

$$f_T = \frac{\sqrt{2 \mu n C_{GS} \frac{W}{L} I_D}}{2\pi C_{GS}} \uparrow$$

(for MOS)