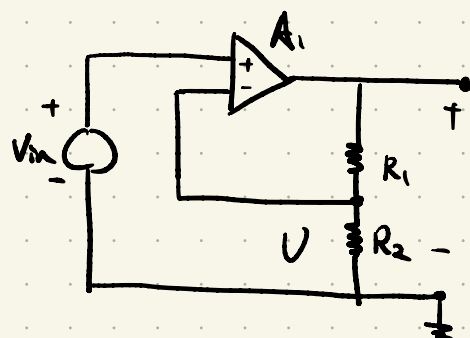


Lec 35

- Example of Voltage-Voltage Feedback
- Application Example

Example




$$\begin{cases} R_1 + R_2 \text{ Very Large} \\ \lambda = 0 \end{cases}$$

$$KA_1 = \frac{g_m R_D R_2}{R_1 + R_2}$$



$$\text{Closed-Loop Input Imp.} = \frac{1}{g_m} \left(1 + \frac{g_m R_D R_2}{R_1 + R_2} \right)$$
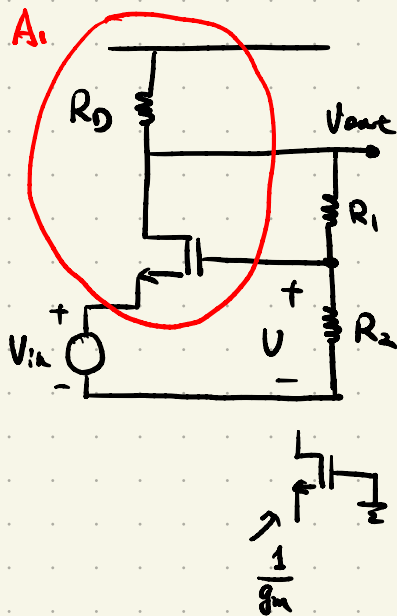
$$\text{Closed-Loop Output Imp.} = \frac{R_D}{1 + \frac{g_m R_D R_2}{R_1 + R_2}}$$




Example

$$\lambda = 0$$

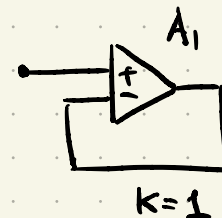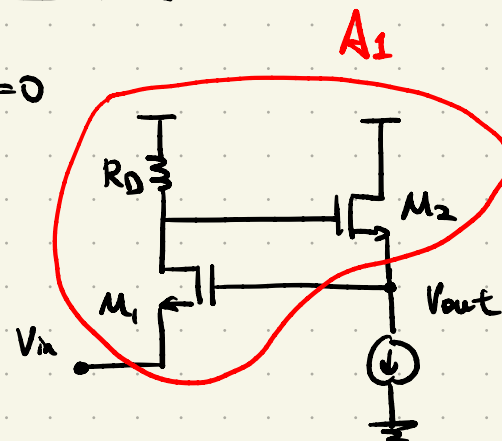


$$\begin{aligned} \text{Closed-Loop Input Imp.} &= \frac{1}{g_{m1}} (1 + A_1) \\ &= \frac{1}{g_{m1}} (1 + g_m R_D) \end{aligned}$$
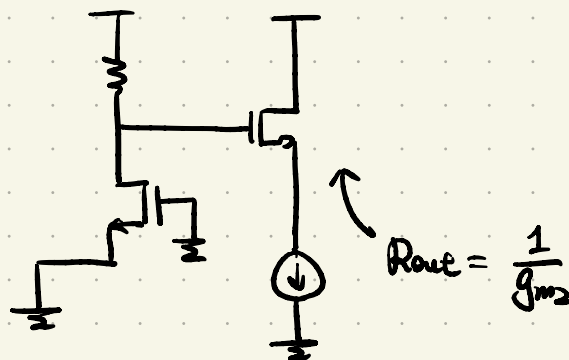
$$\text{Closed-Loop Output Imp.} = \frac{1}{g_{m2}} \frac{1}{1 + g_m R_D}$$




Application Example : Audio Amp

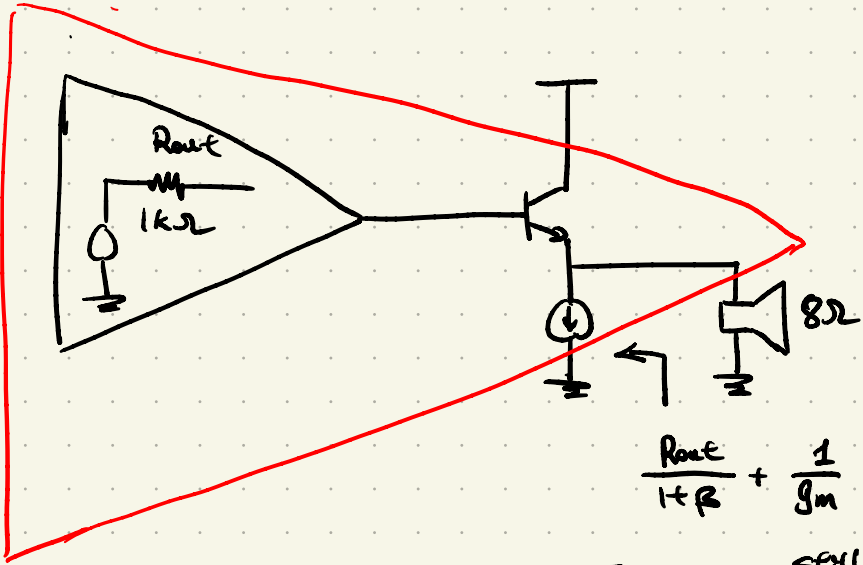

$$\frac{R_{out}}{1 + \beta} + \frac{1}{g_m} > 82$$


still very big

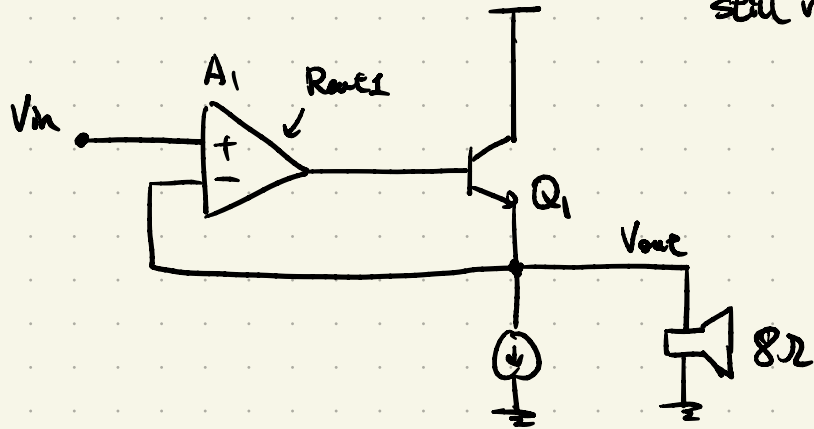


Closed-Loop Output Imp.

$$\frac{\text{Open-Loop Output Imp.}}{1 + \text{Loop gain}} = \frac{\frac{R_{out}}{1 + \beta} + \frac{1}{g_m}}{1 + A_o}$$

Another Perspective:

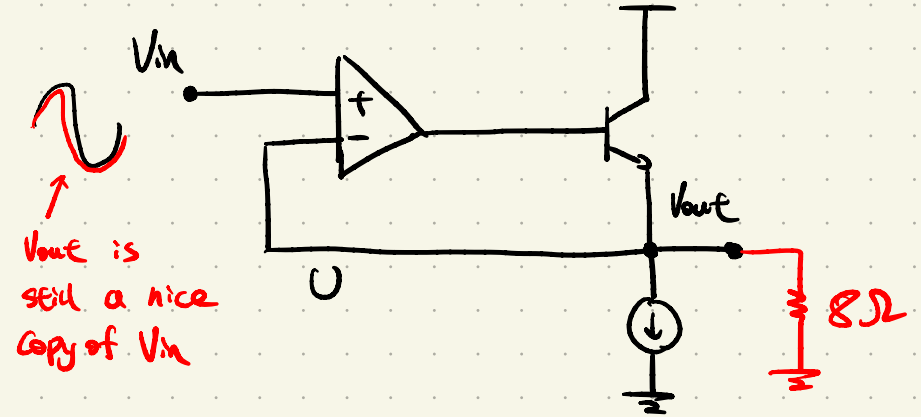


Example How to implement the op amp in the previous example

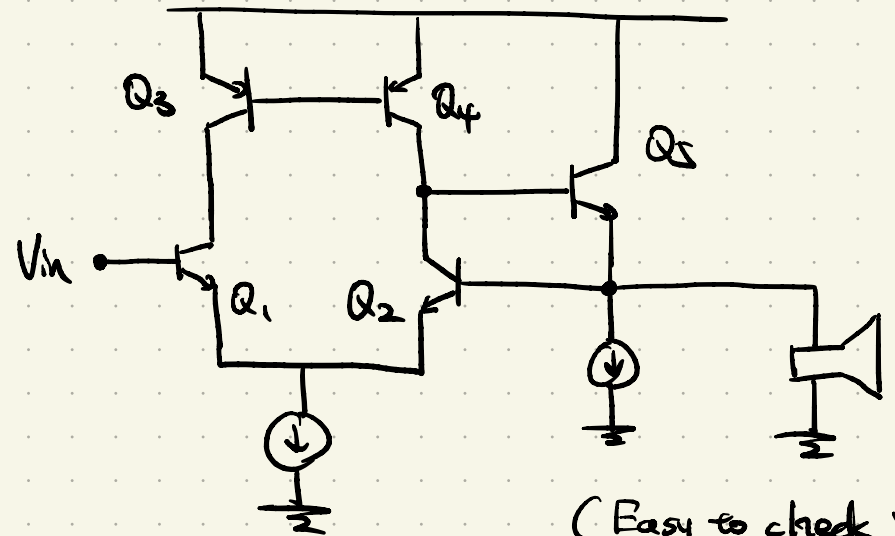
$$A_0 \approx g_{NN} (r_{0N}/r_{op})$$

(Easy to check it is a negative feedback)

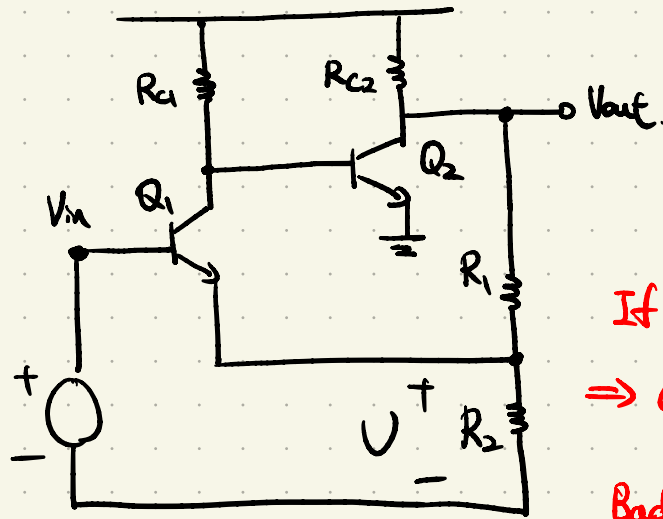Example

Can we use a transistor in the feedback network?



V-V Feedback

If $R_1 + R_2$ is large
 \Rightarrow Good for sensing V_{out}
Bad for returning V

