
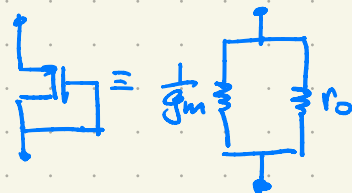


Lec 16

- Small-Signal Behavior of Diff Pair with Active Load

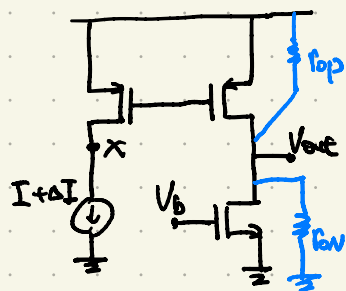Question 1: How much is the voltage change of X?




$$\Delta V_{out} = \Delta I \left(\frac{1}{g_m} \parallel r_O \right) \approx \Delta I \cdot \frac{1}{g_m}$$

Quiz: How much is the change in V_{out} ?

$$A_v = -g_{mp} (r_{on} \parallel r_{op})$$


$$A_v = \frac{\Delta I}{g_{mp}} \times -g_{mp} (r_{on} \parallel r_{op})$$
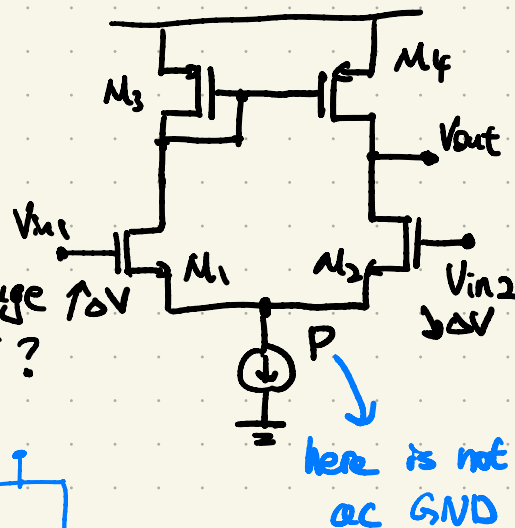
$$= -\Delta I (r_{on} \parallel r_{op})$$



$$\Rightarrow |\Delta V_x| < |\Delta V_{out}|$$

Small-Signal Voltage Gain

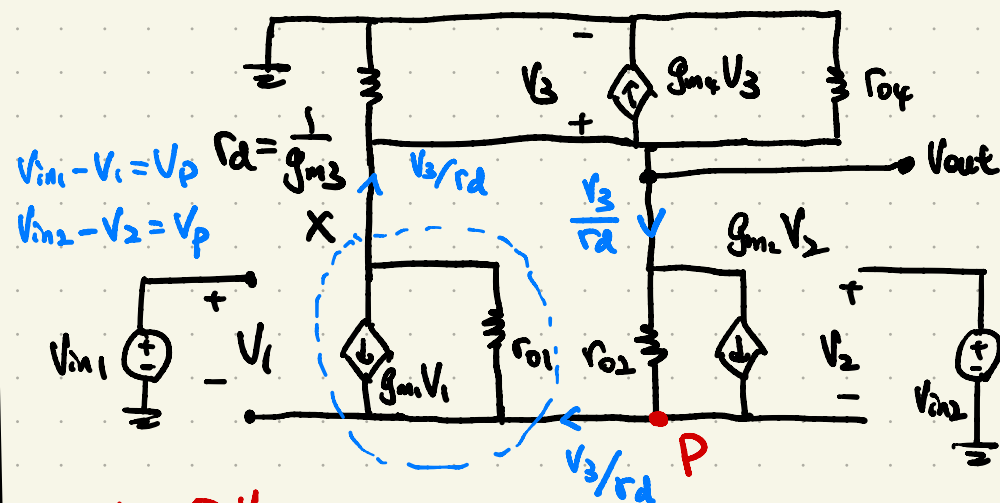

KCL @ V_{out} :

$$\frac{V_3}{r_2} + \frac{V_{out}}{r_{O4}} + g_{m4} V_3 = 0$$

$$V_3 = \frac{-V_{out}}{r_{O4} \left(\frac{1}{r_2} + g_{m4} \right)} = \frac{-V_{out}}{r_{O4} \times (2g_{mp})}$$

$$\text{KCL @ } X: g_{m1} V_1 + \frac{V_3 - V_p}{r_{O1}} + \frac{V_3}{r_2} = 0$$

$$\text{KCL @ Output: } g_{m2} V_2 + \frac{V_{out} - V_p}{r_{O2}} - \frac{V_3}{r_2} = 0$$

$$\Rightarrow g_{mN} (V_1 - V_2) + \frac{V_3 - V_{out}}{r_{on}} + \frac{2V_3}{r_2} = 0$$

$$V_{in1} - V_{in2}$$

$$g_{mN}(V_{in1} - V_{in2}) + \frac{V_3 - V_{out}}{r_{on}} + \frac{2V_3}{r_d} = 0$$

$$V_3 = \frac{-V_{out}}{2g_{mp}r_{op}}$$


Then

$$g_{mN}(V_{in1} - V_{in2}) + \frac{-V_{out}}{2g_{mp}r_{op}r_{on}} - \frac{V_{out}}{r_{on}} - \frac{2V_{out}}{2g_{mp}r_{op}r_d} = 0$$

$$g_{mN}(V_{in1} - V_{in2}) = V_{out} \left[\frac{1}{2g_{mp}r_{op}r_{on}} + \frac{1}{r_{on}} + \frac{1}{r_{op}} \right]$$

$$\frac{V_{out}}{V_{in1} - V_{in2}} = g_{mN}(r_{on} \parallel r_{op})$$

negligible

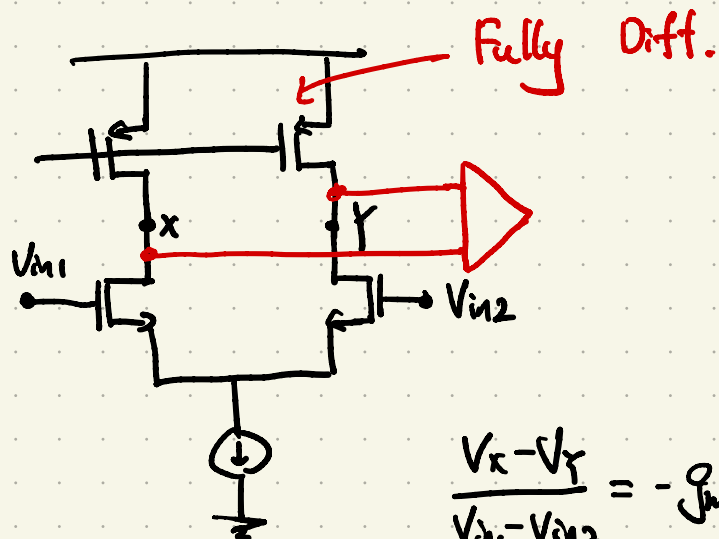

$$\frac{V_x - V_y}{V_{in1} - V_{in2}} = -g_{mN}(r_{on} \parallel r_{op})$$

