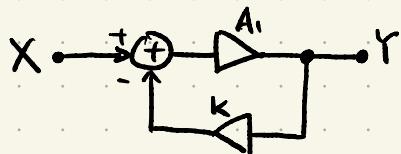


Lec 30 Properties of Negative Feedback

Review of Lec 29

Properties of feedback:



$$\frac{Y}{X} = \frac{A_1}{1 + KA_1}$$

$$\approx \frac{1}{K}$$


(if $KA_1 \gg 1$)

④ Higher Linearity
Impedances

① Gain Desensitization


If A_1 changes due to various factors (temp, supply, freq., load impedance), the closed loop gain does not change as much.

② Bandwidth Extension

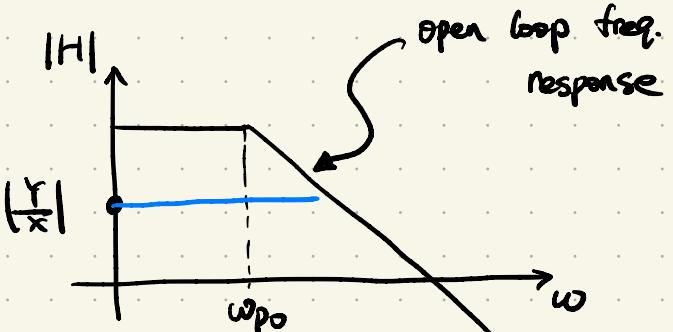

As an example, $A_{\text{L}}(s) = \frac{A_0}{1 + \frac{s}{w_p0}}$
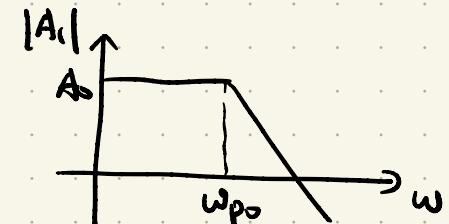
$$\frac{Y}{X}(s) = \frac{\frac{A_0}{1 + \frac{s}{w_p0}}}{1 + K \frac{A_0}{1 + \frac{s}{w_p0}}} = \frac{A_0}{1 + KA_0 + \frac{s}{w_p0}}$$




$$= \frac{A_0}{1 + KA_0 + \frac{s}{w_p0}} = \frac{\frac{A_0}{1 + KA_0}}{1 + \frac{s}{(1 + KA_0)w_p0}}$$

If $s=0 \Rightarrow \frac{Y}{X} = \frac{A_0}{1 + KA_0}$


closed-loop pole:

$$w_p0(1 + KA_0)$$

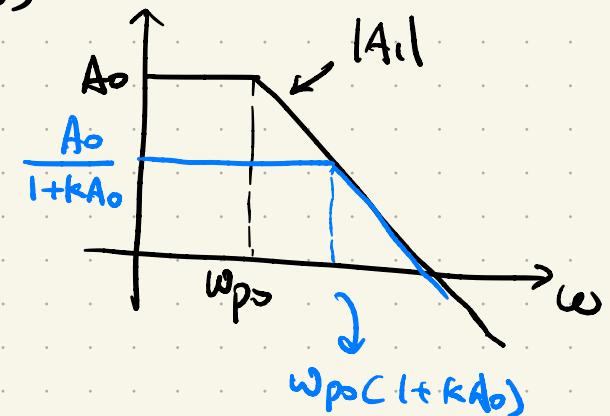

③ Modification of Input and Output Impedances

Without Feedback

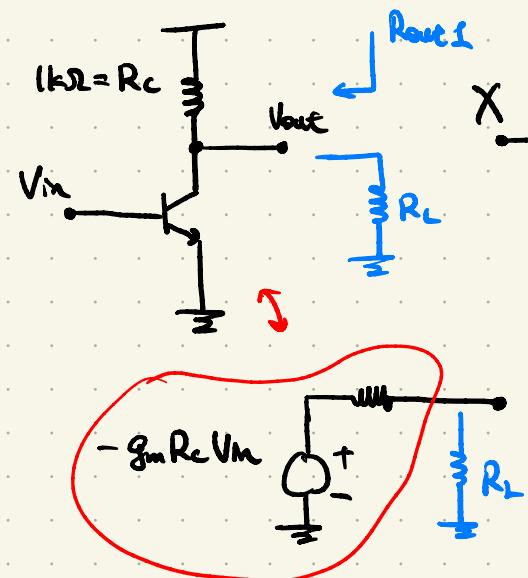

If $R_L = 1k\Omega \Rightarrow$
the gain drops by a factor
of 2 \Rightarrow the output
voltage swing drops by a
factor of 2

without R_L


$$A_V = \frac{\sqrt{5}}{1+5} = 8.33$$

with $R_L = 1k\Omega$

$$A_V = \frac{2\sqrt{5}}{1+2.5} \approx 7.2$$


$A_V = -50$ (without load)

$= -25$ with $R_C = 1k\Omega$

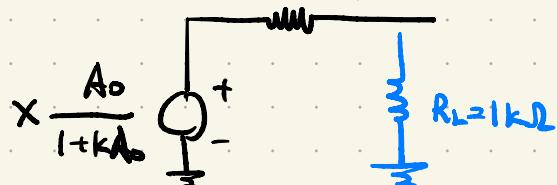

$R_{out2} < R_{out1}$

④ Higher Linearity

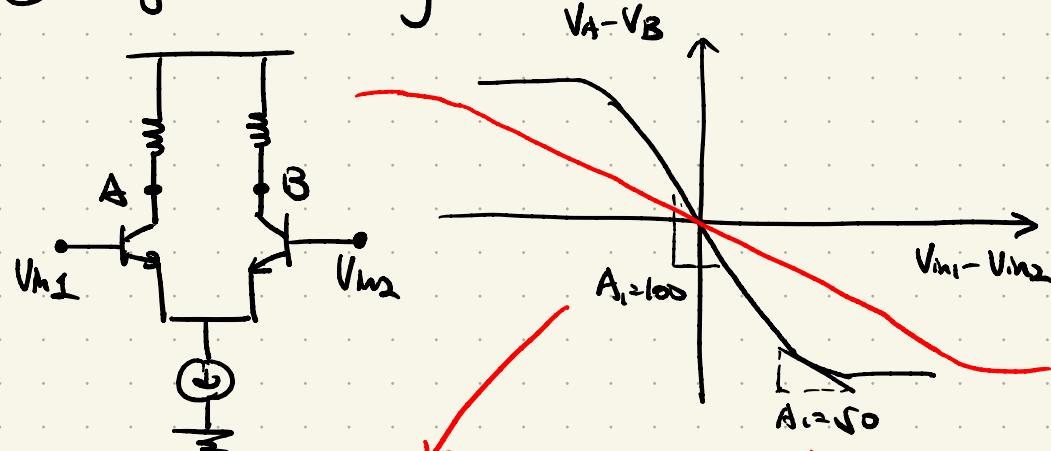

closed-loop gain

$$= \frac{A_1}{1+KA_1} = 9.1$$



closed-loop gain

$$= \frac{A_1}{1+KA_1} = 8.33$$


Prerequisites for Analysis of feedback Circuits.

- A few Quick Notes


- (a) Ideal vs. Real Sources

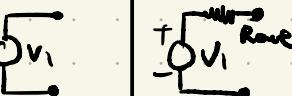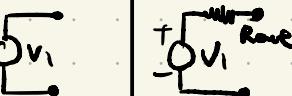	Ideal	Real
Voltage source		
Current Source		

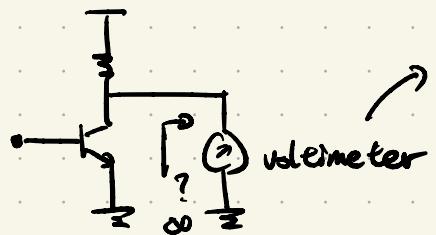- (b) How do we measure a voltage or a current?



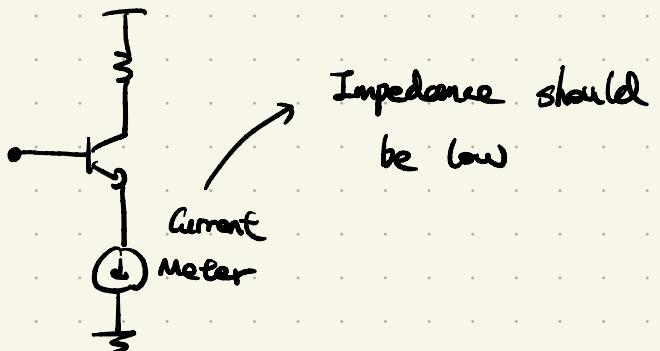any device or circuit that measures voltage must have a high Impedance



Impedance should be low