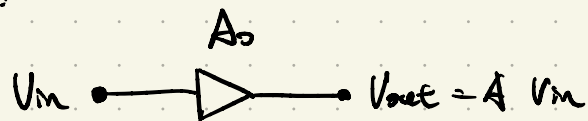



# Lec 8.

- Intuitive study of Bipolar Differential Pair
- Common mode and Differential characteristics.


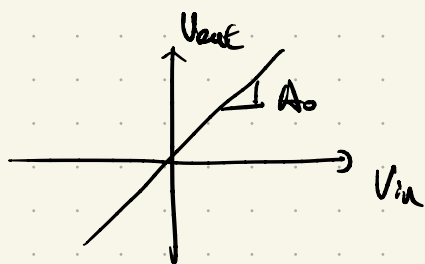
Example:



Construct the input-output relationship of this circuit.




slope = gain

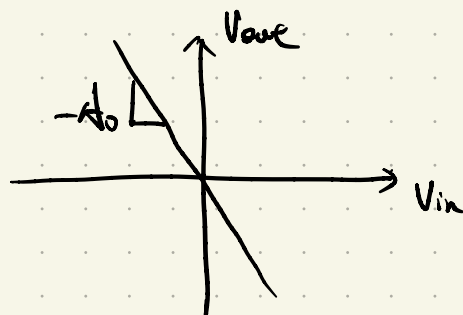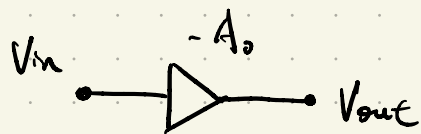

- Bipolar Differential Pair

Case I:

$I_{C1}, I_{C2}, V_x, V_y$  ?

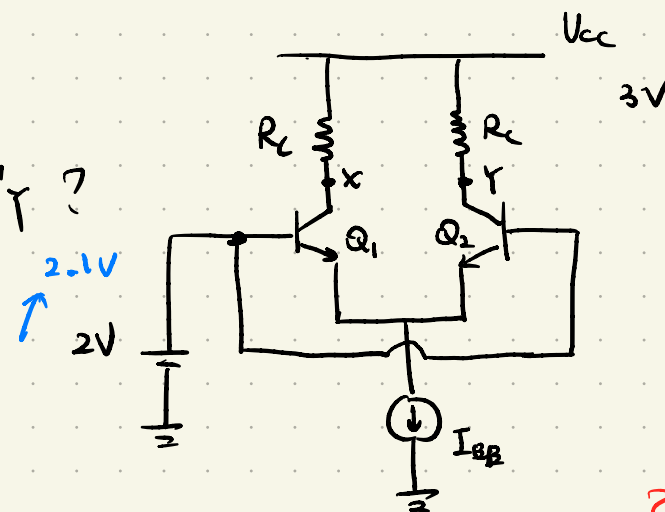

Due to symmetry

$$I_{C1} = I_{C2} = \frac{1}{2} I_{EE}$$

$$V_x = V_y = V_{ce} - \frac{1}{2} I_{EE} R_c$$

The differential pair rejects perturbations in the input common mode level


⇒

If  $V_{in1} - V_{in2} = 0$  then  $V_x - V_y = 0$

Differential Input Voltage

Differential Output Voltage

Q

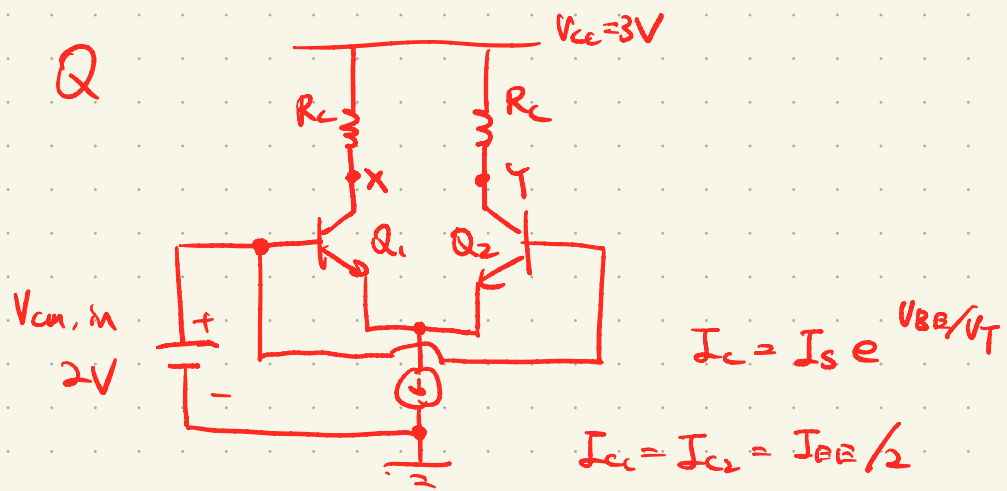


$$I_C = I_S e^{V_{BE}/V_T}$$

$$I_{C1} = I_{C2} = I_{EE}/2$$

$$V_X = V_{CC} - \frac{1}{2} I_{EE} R_C$$

$$V_Y = V_{CC} - \frac{1}{2} I_{EE} (R_C + \Delta R)$$

Case II:

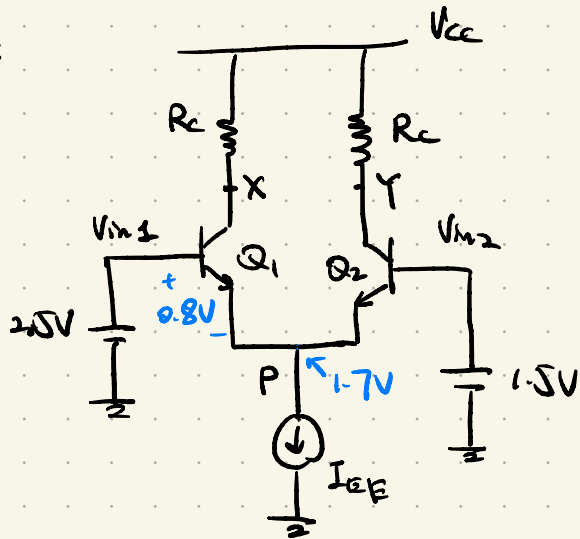

Guess:  $Q_1$  is on and has some current

$$\Rightarrow V_P = 2.5 - 0.8 = 1.7V \Rightarrow Q_2 \text{ off}$$

then

$$I_{C1} = I_{EE} \quad I_{C2} = 0$$

then  $V_X = V_{CC} - R_C \cdot I_{EE}$

$$V_Y = V_{CC}$$

$\Rightarrow V_X - V_Y$  is a function of  $V_{in1} - V_{in2}$

Case III

$$V_{in1} = 1.5V, \quad V_{in2} = 2.5V$$

$$\Rightarrow I_{C1} = 0 \quad I_{C2} = I_{EE}$$

$$V_X = V_{CC}, \quad V_Y = V_{CC} - I_{EE} R_C$$

First, Input-Output charac.

