
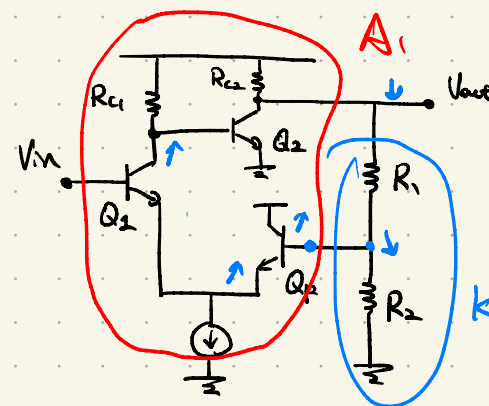


Lec 36

- Additional Examples of Voltage-Voltage Feedback
- Summary of Voltage-Voltage Feedback Circuits

Example

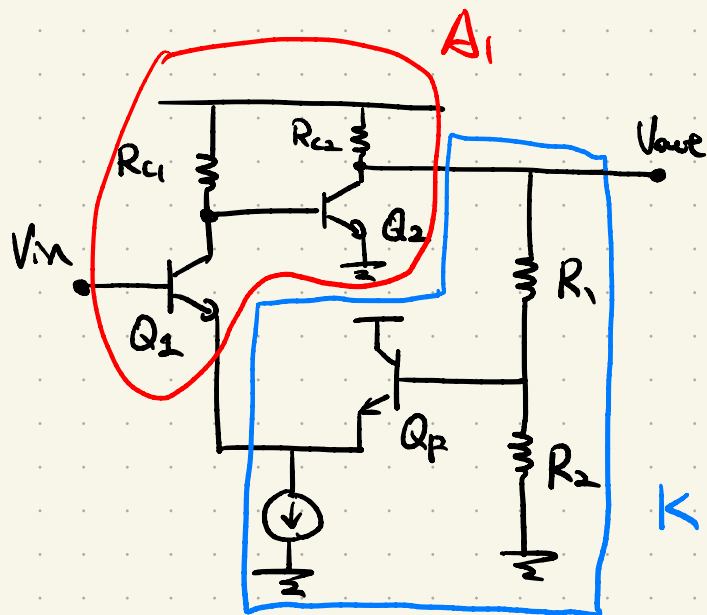


Negative feedback

$R_1 + R_2 = \text{large}$

$V_A = \infty$

① Find the open-loop parameters

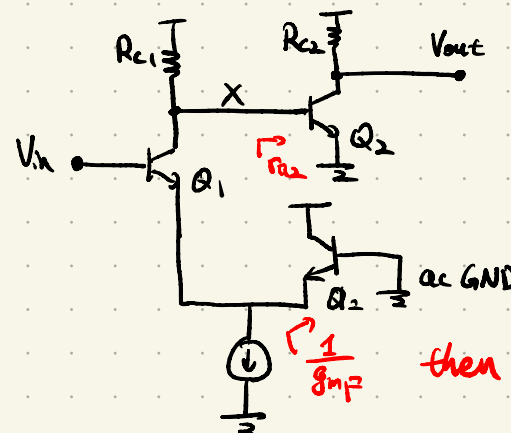

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{X} \cdot \frac{X}{V_{in}}$$

$$\frac{V_{out}}{X} = -g_{m2} R_{c2}$$

$$A_1 = \frac{R_{c1} / R_{c2}}{1/g_{m1}} \times g_{m2} R_{c2}$$

$$\frac{X}{V_{in}} = - \frac{R_{c2} \parallel R_{c1}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \quad (g_{m1} \approx g_{m2})$$

$$\text{Closed-Loop Gain} = \frac{A_1}{1 + K A_1}$$

$$K \approx \frac{R_2}{R_1 + R_2}$$

$$R_{in} = r_{\pi 1} + (\beta + 1) \frac{1}{g_{m1}}$$



$$= 2r_{\pi 1}$$

$$R_{out} = R_{c2}$$

$$\text{CL Input Imp.} = 2r_{\pi 1} (1 + K A_1)$$


$$\text{CL Output Imp.} = \frac{R_{c2}}{1 + K A_1}$$

Example

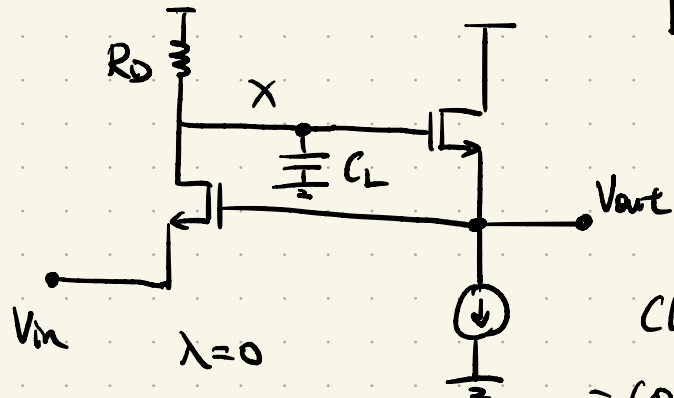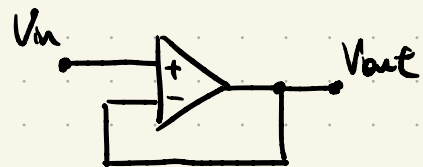

Closed-Loop BW
= (Open-Loop BW)
(1 + loop gain)
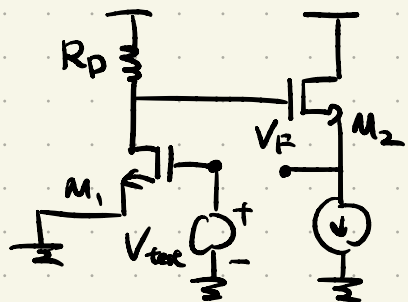
$$\text{Open-Loop BW} = \text{Pole Freq} = \frac{1}{R_O C_L} = \omega_p$$







$$\frac{V_R}{V_{out}} = -g_{m1} R_O$$

$$\text{loop gain} = g_{m1} R_O$$


$$g_{m1} R_O \gg 1$$

$$\text{Closed-Loop BW} = \frac{1}{R_O C_L} (1 + g_{m1} R_O) \approx \frac{g_{m1}}{C_L}$$

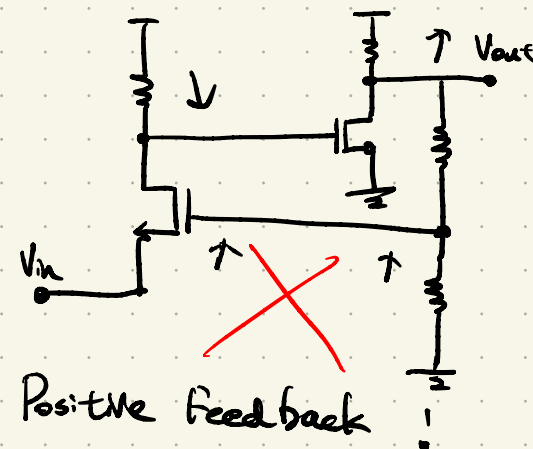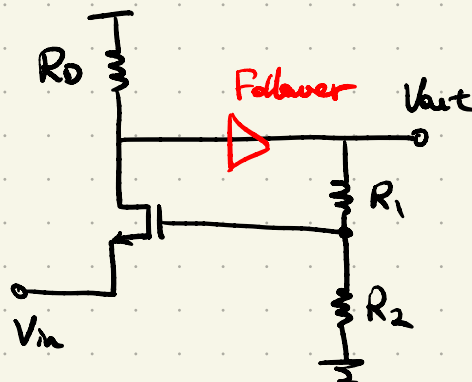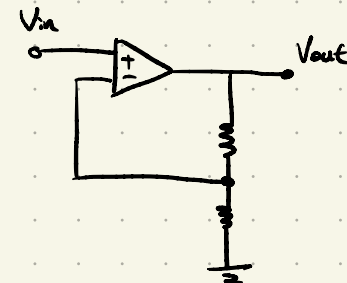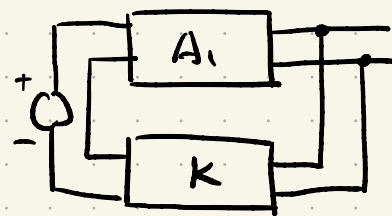Summary of Voltage-Voltage Feedback Circuits



Positive Feedback !

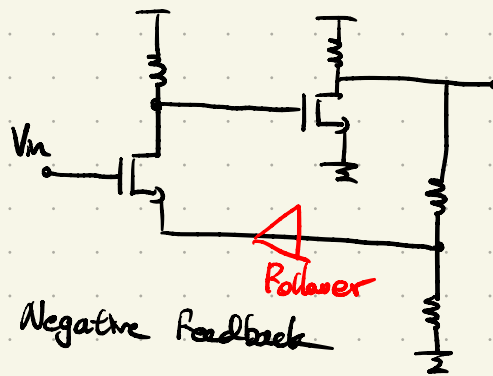

Negative Feedback

