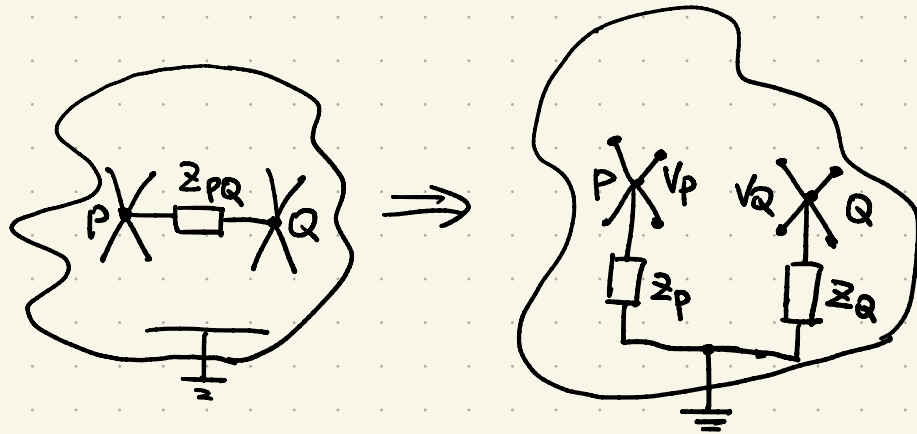


Lec 19

- The Miller Effect
- High-freq. Model of Bipolar Transistor

• Miller's Theorem




Current drawn from P: $\frac{V_p - V_Q}{Z_{pQ}} = \frac{V_p}{Z_p}$

$$Z_p = \frac{Z_{pQ}}{1 - \frac{V_Q}{V_p}}$$

$$Z_Q = \frac{Z_{pQ}}{1 - \frac{V_p}{V_Q}}$$

Example

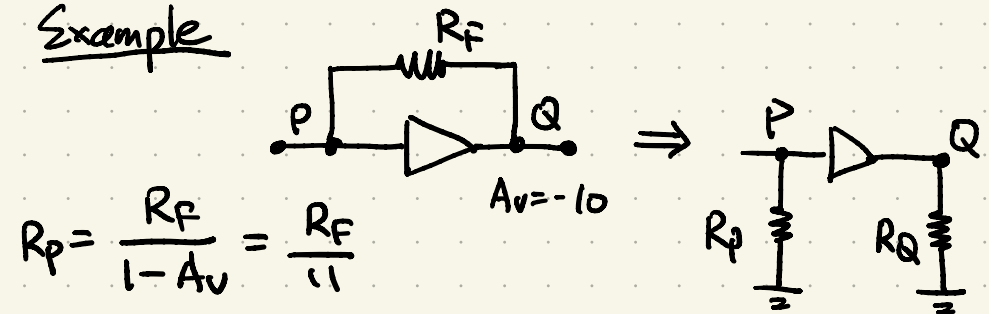

$$R_p = \frac{R_f}{1 - A_v} = \frac{R_f}{11}$$

$$R_Q = \frac{R_f}{1 - \frac{1}{A_v/V_p}} = \frac{R_f}{1.1}$$



The Miller Effect: Z_{pQ} is divided by $1 - A_v$ as it appears at the input.

Q: What if


$$A_v = +10V$$

$$R_p = \frac{R_f}{-9}$$

Example

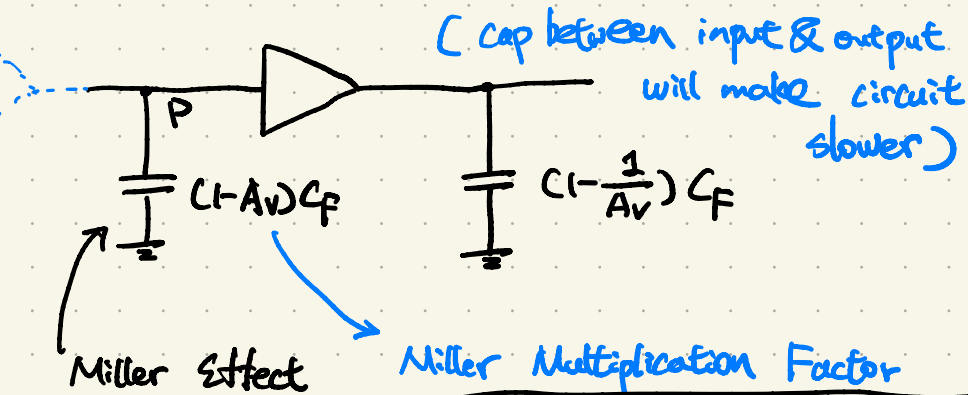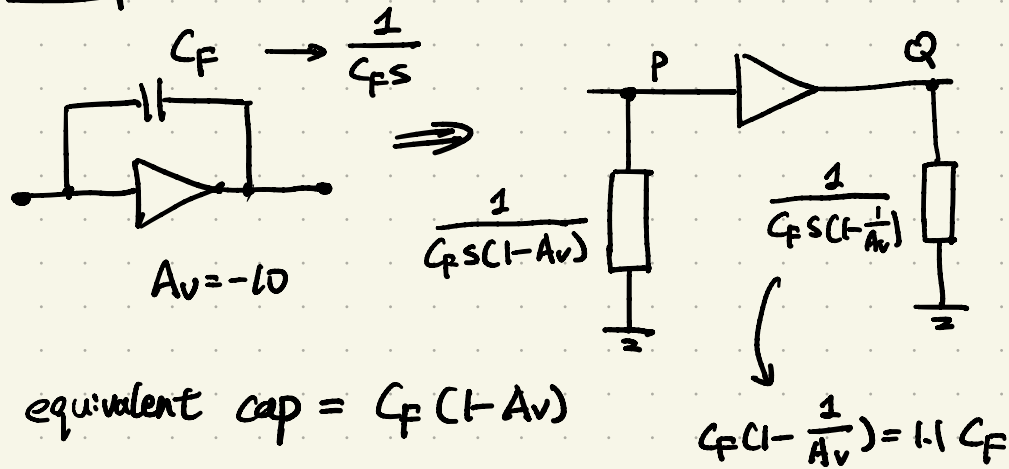

Example

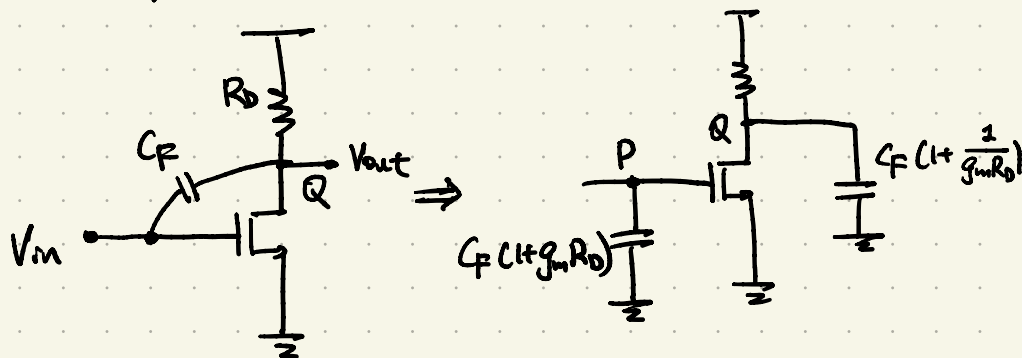

Caution: ① Miller's approximation has introduced new pole!
(because we assume the A_v to be low-freq. gain)

② Miller's approximation has eliminate the zero

High-Freq. Model of Bipolar Transistors

