
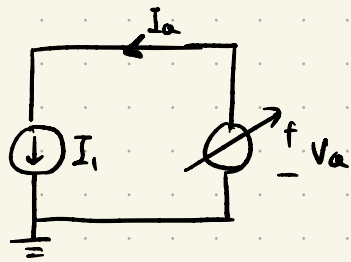


# Lec 1. Introduction, Cascode Current sources

## Cascode current source



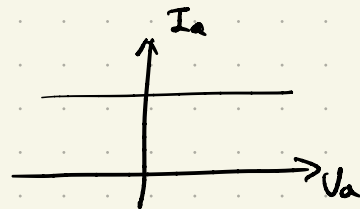


Ideal current source



## Observations




### ① Let's build a current source

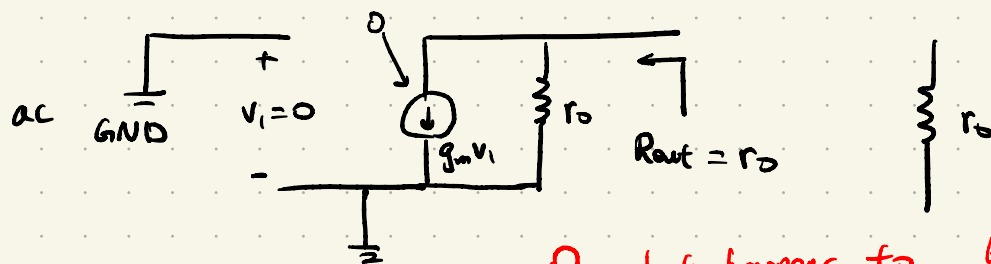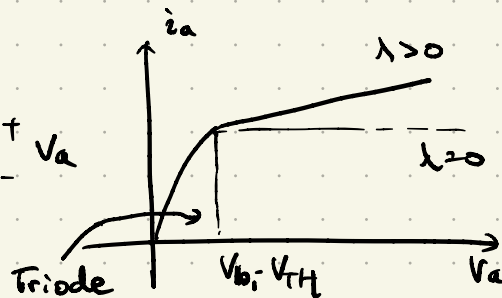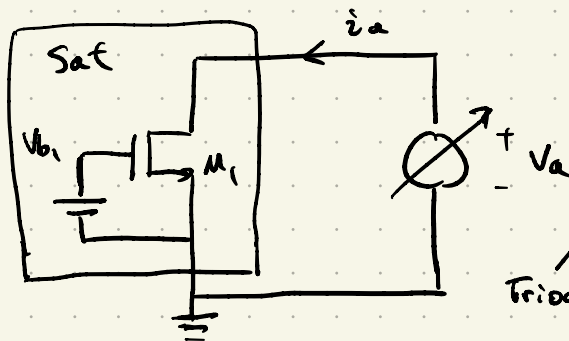

A:  $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$   
 $\Rightarrow R_{out}' = \sqrt{2} R_{out}$


Q: what happens to  $R_{out}$  if width  $W_1, W_2$  are doubled? (to the same)
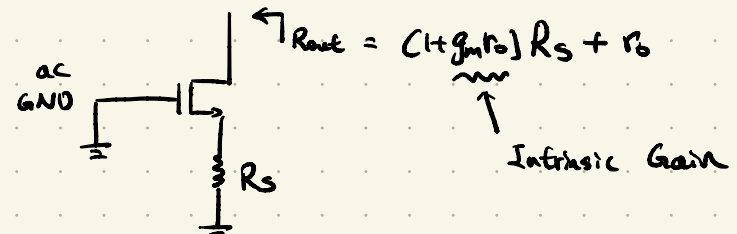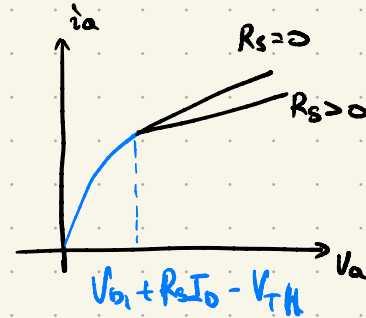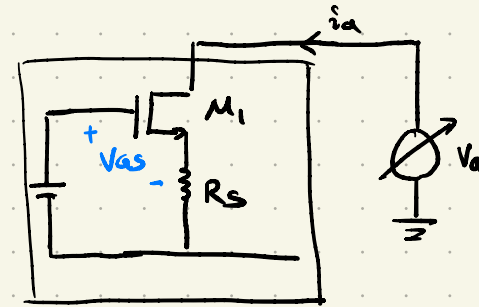
### ② How do we improve this current source



degeneration, slope  $\downarrow$  but range  $\downarrow$

### ③ Cascode current source

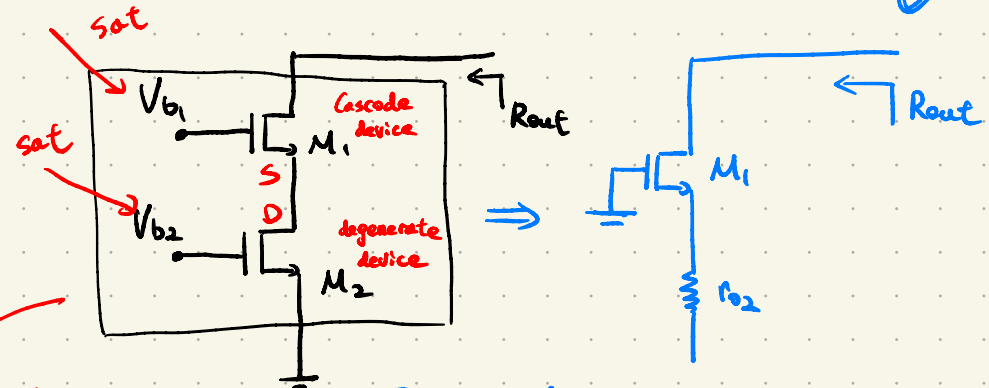

$$R_{out} = (1 + g_{m1} r_{o1}) r_{o2} + r_{o1} \approx g_{m1} r_{o1} r_{o2}$$

$\phi$   $M_2$  degen.  $M_1$   
 $\Leftrightarrow M_1$  increases the  $r_o$  of  $M_2$