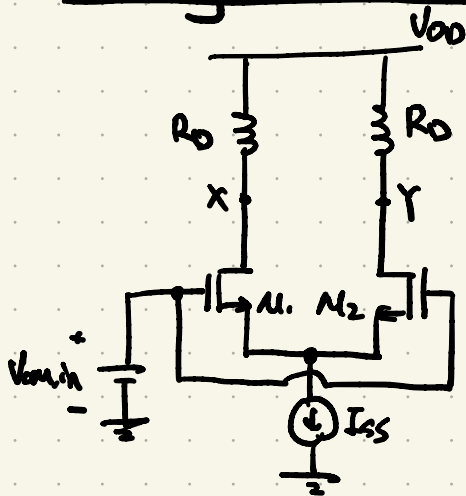


# Lec 13

- Detailed Analysis of MOS Diff. Pair's Large-Signal Response

- Overall Input-Output Characteristic
- Dependencies on Various Parameters

## Summary of the Results



$$V_X - V_Y = -R_D (I_{D1} - I_{D2})$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

$$V_{GS} - V_{TH} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

Equilibrium Overdrive

②


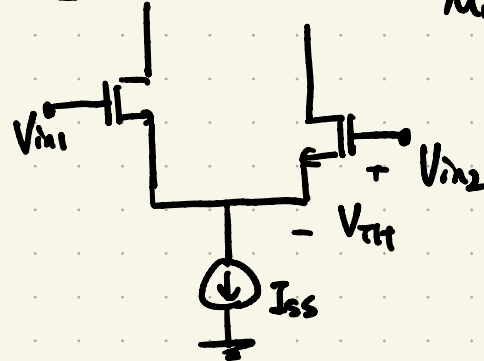


Min  $|V_{in1} - V_{in2}|$  necessary

to turn off one side:

$$\sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

③

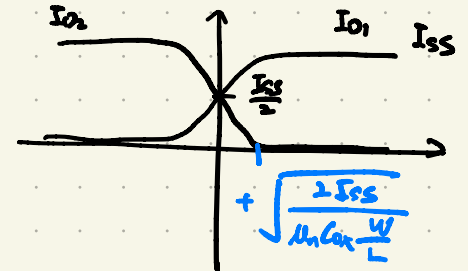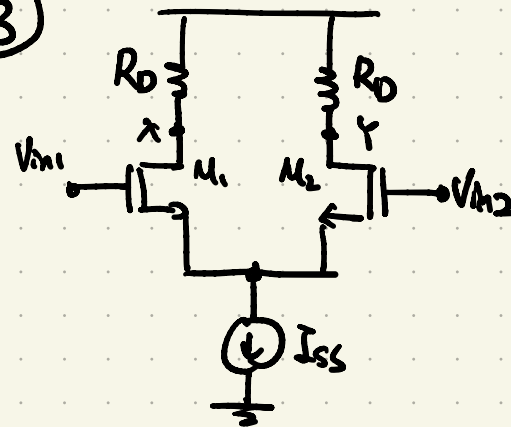

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$


valid if  $M_1$  and  $M_2$  are on or near turning off

• If  $V_{in1} - V_{in2} = 0 \Rightarrow I_{D1} = I_{D2}$

• This equation is valid only if  $|V_{in1} - V_{in2}| \leq \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$

Minimum  $|V_{in1} - V_{in2}|$  to turn off one side =  
 $\sqrt{2} \times \text{Equilibrium Overdrive Voltage}$
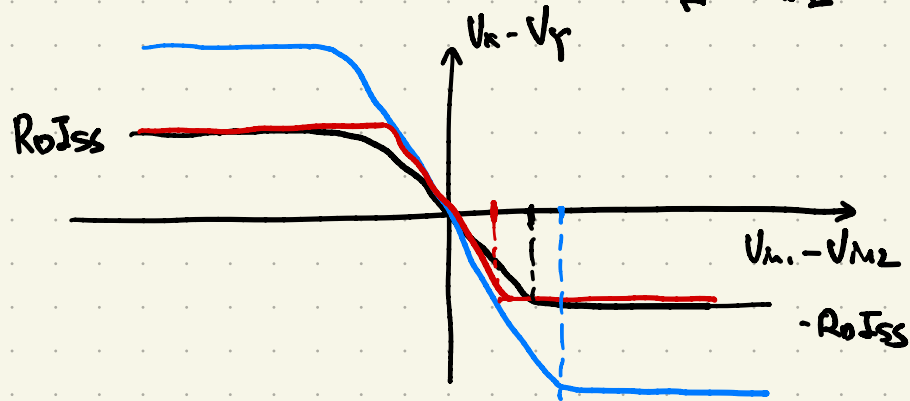
$$\textcircled{14} \quad V_K - V_T = -\frac{R_D}{2} \ln \coth \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4 I_{SS}}{\ln \coth \frac{W}{L}}} (V_{in1} - V_{in2})^2$$



$$\text{If } (V_{in1} - V_{in2})^2 \ll \frac{4 I_{SS}}{\ln \coth \frac{W}{L}}$$

$$\Rightarrow V_K - V_T \approx -\frac{R_D}{2} \ln \coth \frac{W}{L} \sqrt{\frac{4 I_{SS}}{\ln \coth \frac{W}{L}}}$$

$$= -\sqrt{\ln \coth \frac{W}{L} I_{SS}} R_D (V_{in1} - V_{in2})$$

$$\text{The Slope} = -\sqrt{\ln \coth \frac{W}{L} I_{SS}} R_D$$

Example

What happens if  $I_{SS}$  is doubled?  
blue line

- Slope' =  $\sqrt{2}$  slope
- The circuit becomes more linear because it can take a larger input difference without "dying"

Quiz: What happens if  $\frac{W}{L}$  is doubled?  
red line

The circuit become less linear