

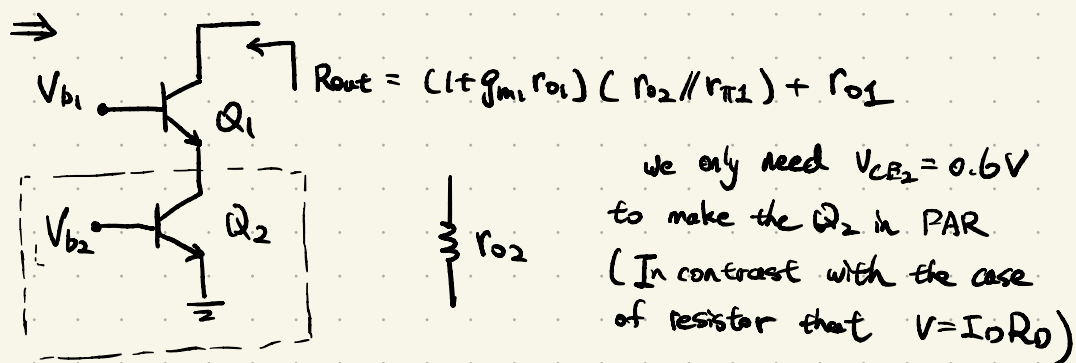


Lec 2. Mos and Bipolar Cascode Current source, Intro. to Cascode Amplifiers

Bipolar Cascode Current Sources

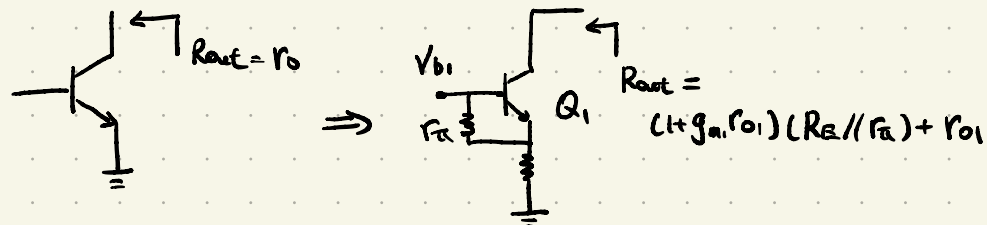

Example

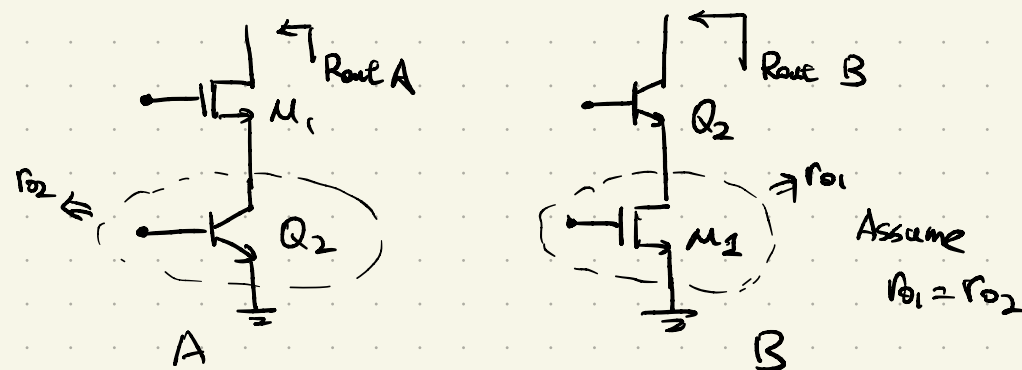

$$R_{out A} = (1 + g_{m1} r_{o1}) r_{o2} + r_{o1}$$

$$\approx g_{m1} r_{o1} r_{o2}$$





$$R_{out B} = (1 + g_{m2} r_{o2})(r_{o1} // r_{\pi 2}) + r_{o2}$$

$$\approx g_{m2} r_{o2} (r_{o1} // r_{\pi 2})$$


For a given bias current:

$$g_{m, MOS} < g_{m, BJT}$$


P-Type Current Sources

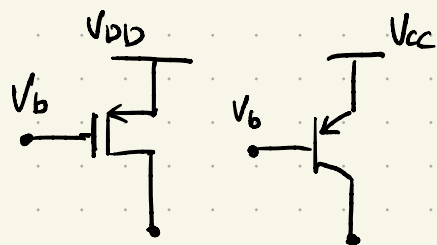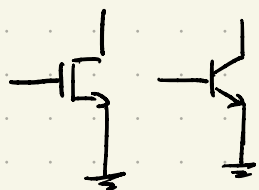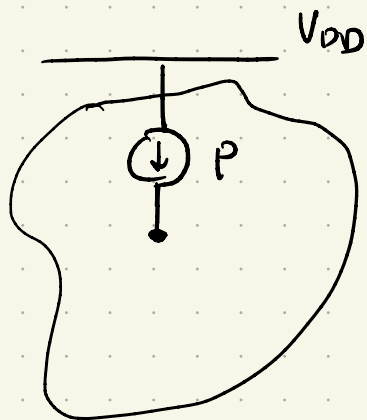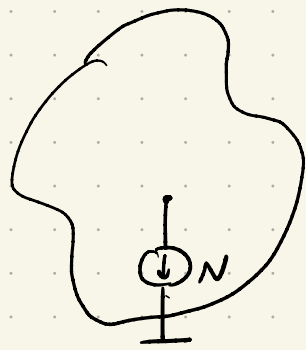


P-Type Cascodes

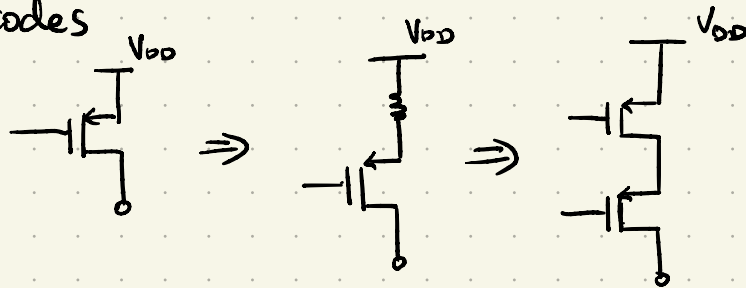

N-Type Cascodes

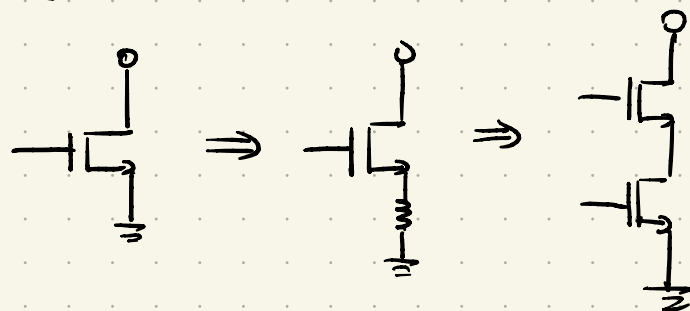


P-Type BJT Cascode

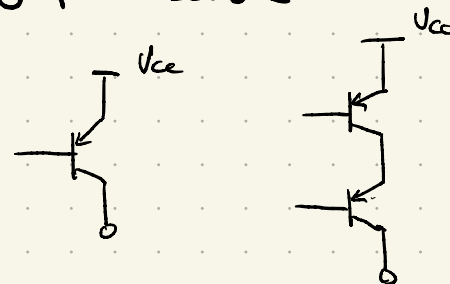

Intro. to Cascode Amplifiers


Observations

① Transconductance for General Circuit

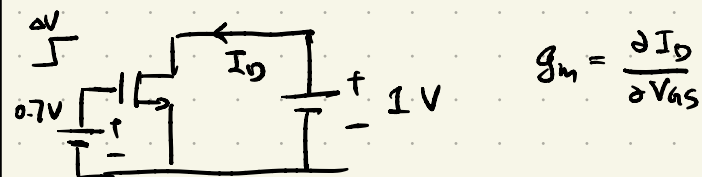



$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

⇒ Small Signal Model:

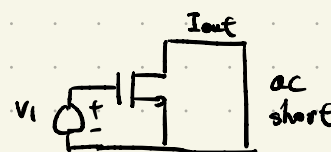


$$g_m = \frac{i_{out}}{V_i}$$

General Linear Circuit

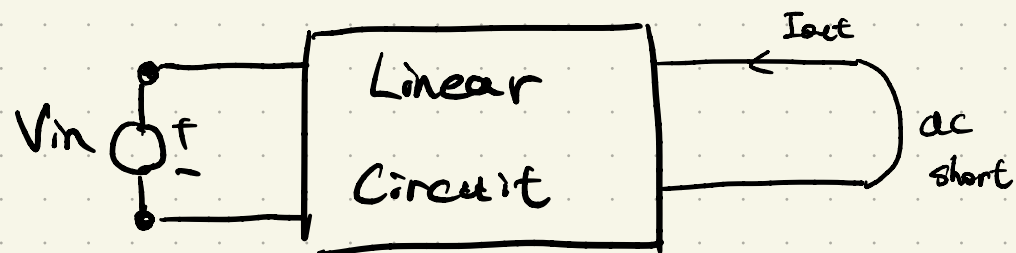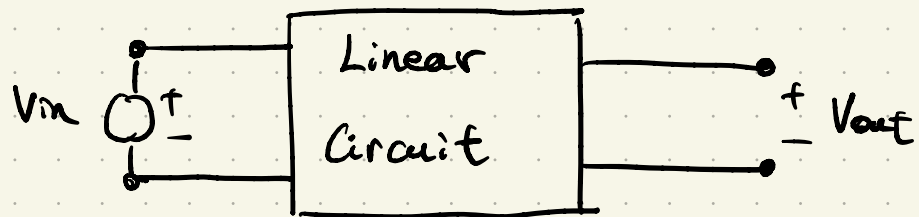


$$G_m = \frac{I_{out}}{V_{in}}$$

Voltage Gain

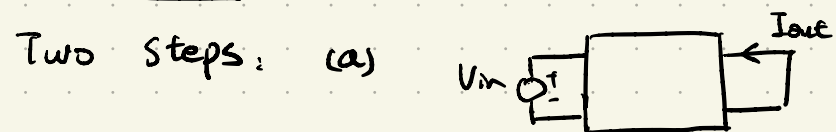


$$G_m = \frac{I_{out}}{V_{in}}$$

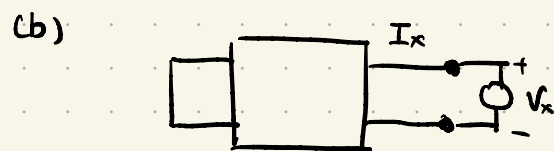

$$R_{out} = \frac{V_x}{I_x}$$


$$A_v = \frac{V_{out}}{V_{in}} = -G_m R_{out}$$

Example

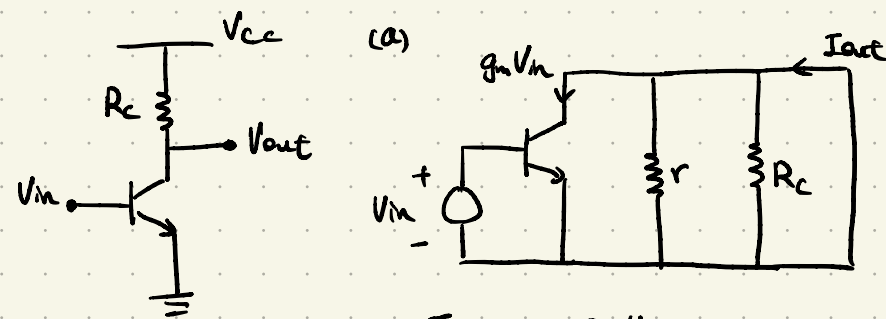

$$G_m = \frac{I_{out}}{V_{in}} = \frac{g_m V_{in}}{V_{in}} = g_m$$

(b)

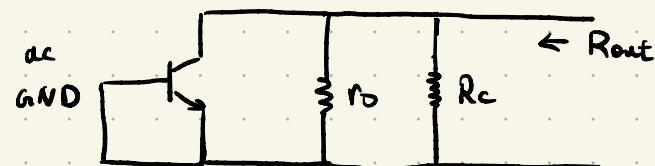

$$R_{out} = r_o \parallel R_c$$

then

$$A_v = -g_m (r_o \parallel R_c)$$