
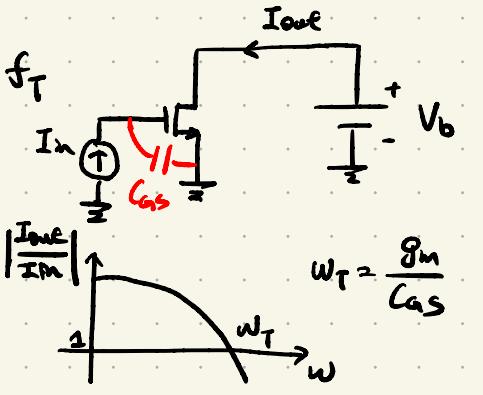


## Lee 26 Additional freq. Resp. Examples


- MOS Cascade
  - CS Stage with Current-Source Load
  - Cascaded Stages
  - $f_T$  Revisited

## Review of Lec. 25

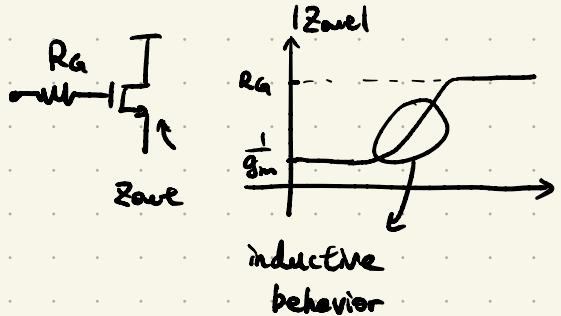

## Mos Cascade

Find poles by inspection

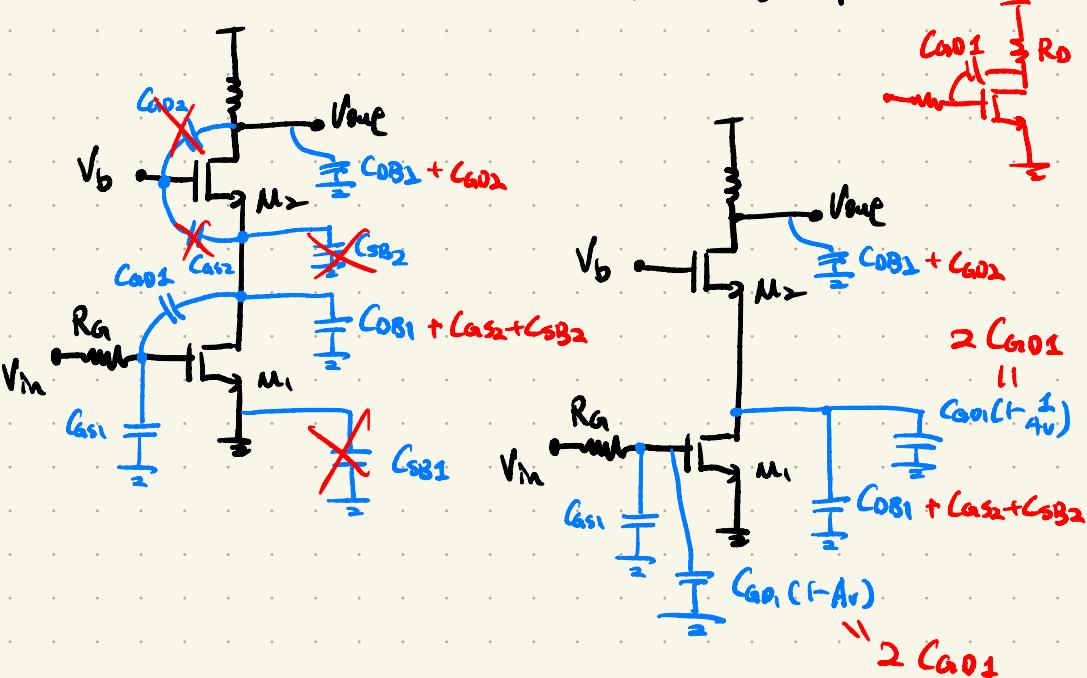

$$A_V = \frac{V_B}{V_A} = -g_{m1} \times \frac{1}{g_{m2}} = -\frac{\sqrt{2} \ln(\cos(\frac{\omega}{L})_2 I_{D1}}}{\sqrt{2} \ln(\cos(\frac{\omega}{L})_2 I_{D2}}}$$

In most cases  $(\frac{w}{L})_1 = (\frac{w}{L})_2$

$$\Rightarrow A_V = 1$$


(lower Miller multi.)  
compare to (S amp.)



$$\omega_{p,A} = \frac{1}{R_A(C_{AS1} + 2C_{G01})}$$

$$W_{p,B} = \frac{1}{\frac{1}{g_{m_2}}(C_{031} + C_{052} + C_{SB2} + 2C_{01})}$$

$$W_{p,out} = \frac{1}{R_A C (C_{AO_2} + C_{OB_2})}$$

- CS stage with current - source load

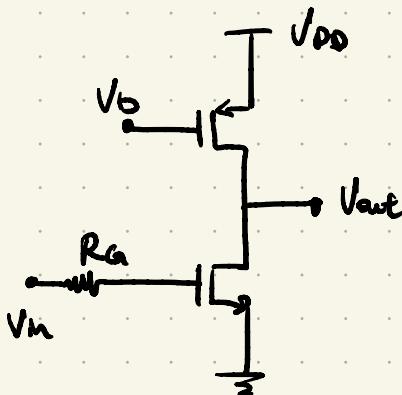

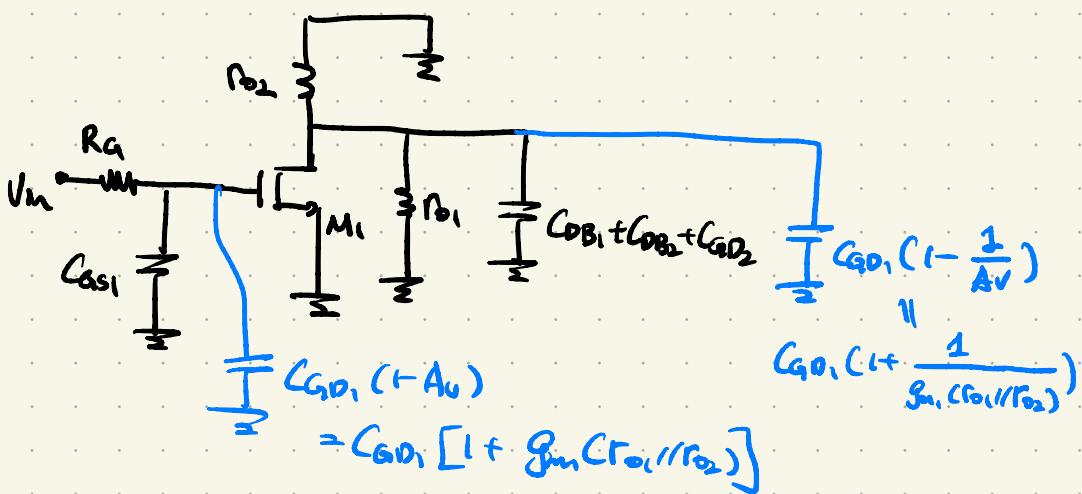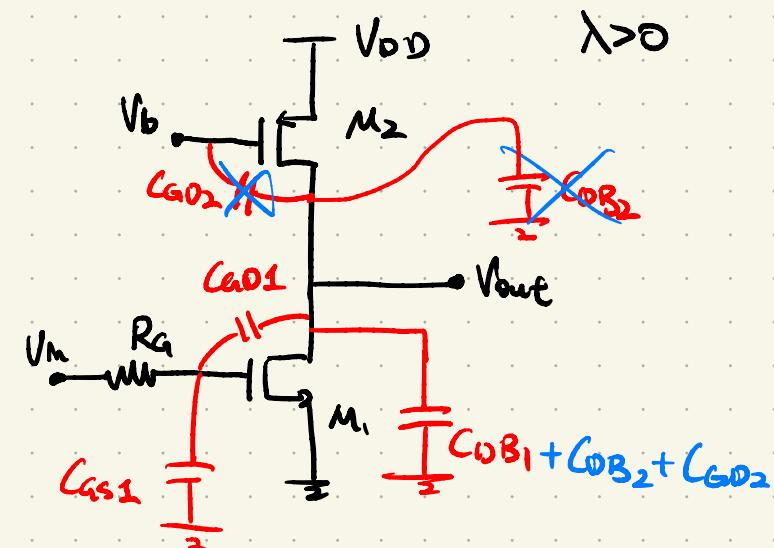


$$W_{p,m} = \frac{1}{R_{G_1} (C_{GS1} + C_{GD_1} [1 + g_m(R_{D1}/r_{D2})])}$$

$$W_{p,out} = \frac{1}{(F_{O_2}/P_{O_2}) \left[ C_{O_2} + C_{OB_2} + C_{GO_2} + C_{Ga} \left( 1 + \frac{1}{g_m(F_{O_2}/P_{O_2})} \right) \right]}$$

## Example

## Cascaded Stages

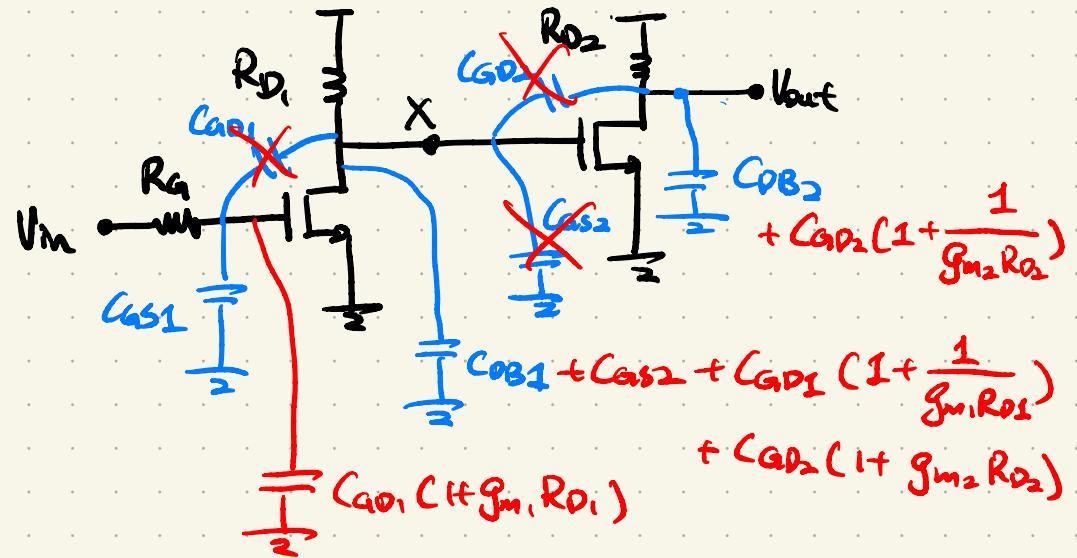

$$W_{p,m} = \frac{1}{[C_{GS,1} + C_{GD,1}(1+g_m(R_{D,1}))]R_q}$$

$$w_p, x = \frac{1}{R_{D1} [ C_{DB1} + C_{AS1} + C_{GD1} \left( 1 + \frac{1}{g_{m1} R_{D1}} \right) + C_{GD2} \left( 1 + g_{m2} R_{D2} \right) ]}$$

$$w_{p,\text{out}} = \frac{1}{R_{02} [C_{DB_2} + C_{GD_2} \left(1 + \frac{1}{g_{m2} R_{02}}\right)]}$$

## $f_T$ Revisited

$$f_T = \frac{g_m}{2\pi C_{as}} = \frac{\sqrt{2Lm \cos \frac{w}{2} I_D}}{2\pi C_{as}}$$

what happens if  $\frac{w}{2}$  is doubled?

(a)  $I_D$  is constant?

$$f_T \rightarrow \frac{f_T}{\sqrt{2}}$$

(b)  $I_D$  is doubled

$$f_T \rightarrow f_T$$

$$g_m \rightarrow 2g_m$$

$$C_{as} \rightarrow 2C_{as}$$