
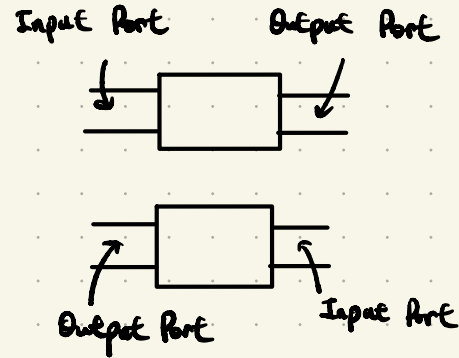


# Lec 32


- Sense & Return Mechanisms
- Feedback Circuit Examples

## Alternative Feedback Model

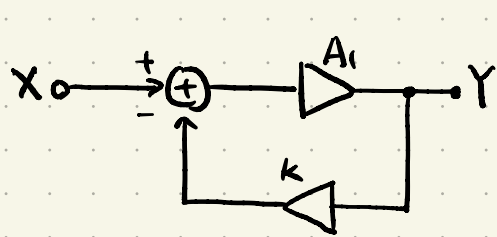


## Sense Mechanisms

### Voltage

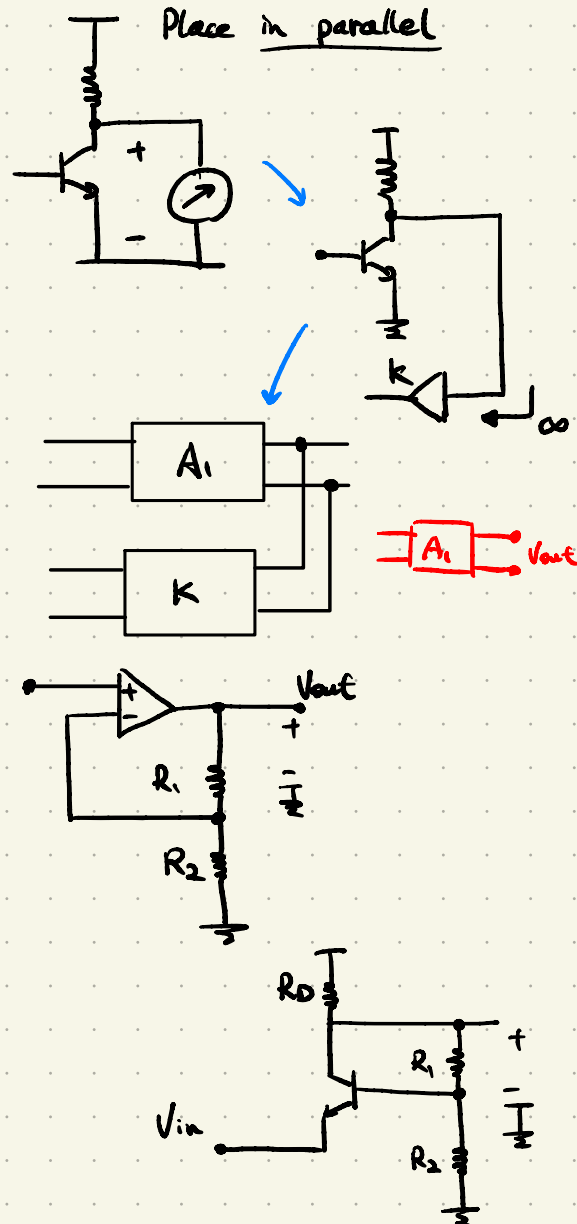




### Current

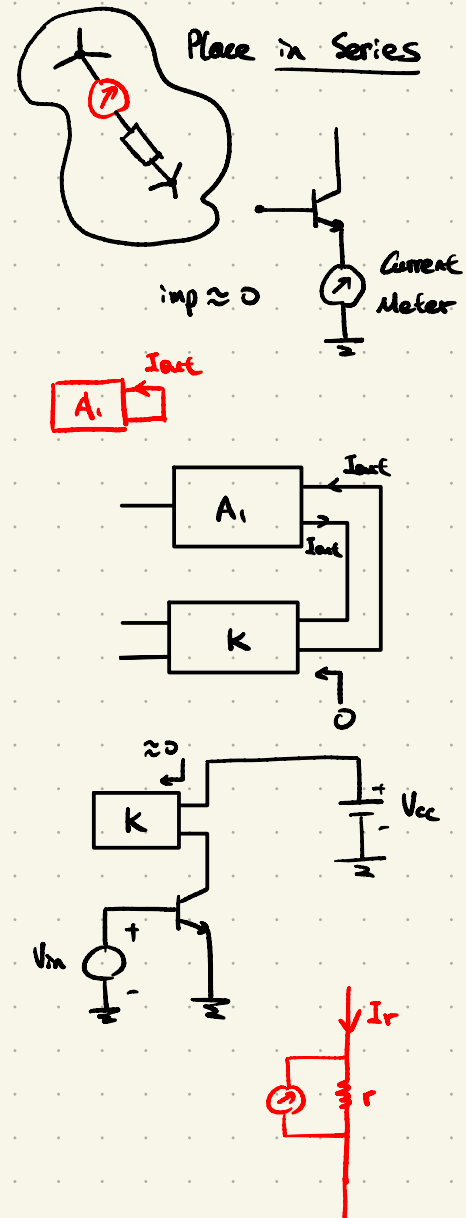




# Return Mechanisms

How to subtract two voltages or two currents?

Voltage

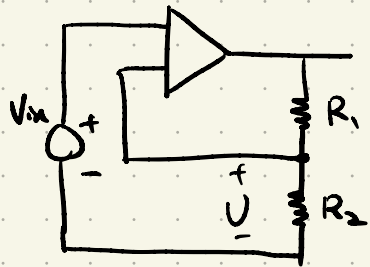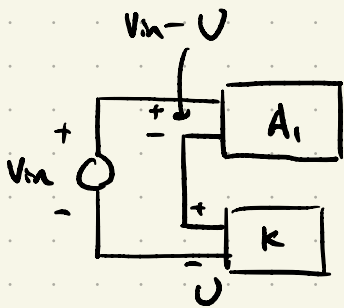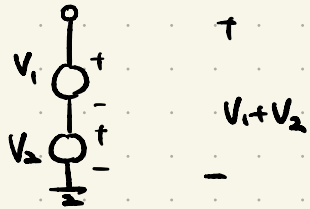

Current

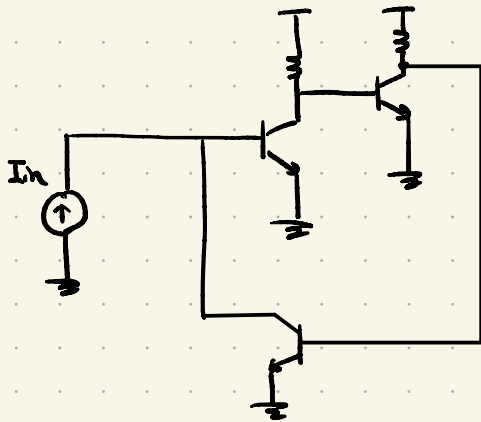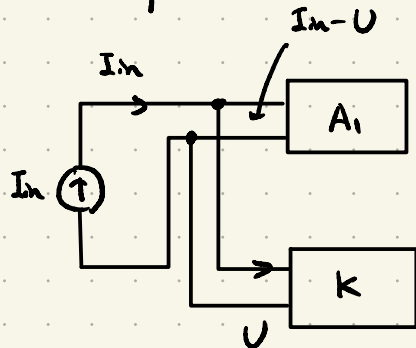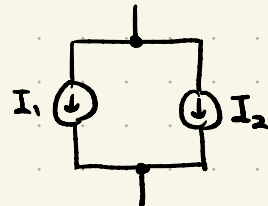

## Examples

