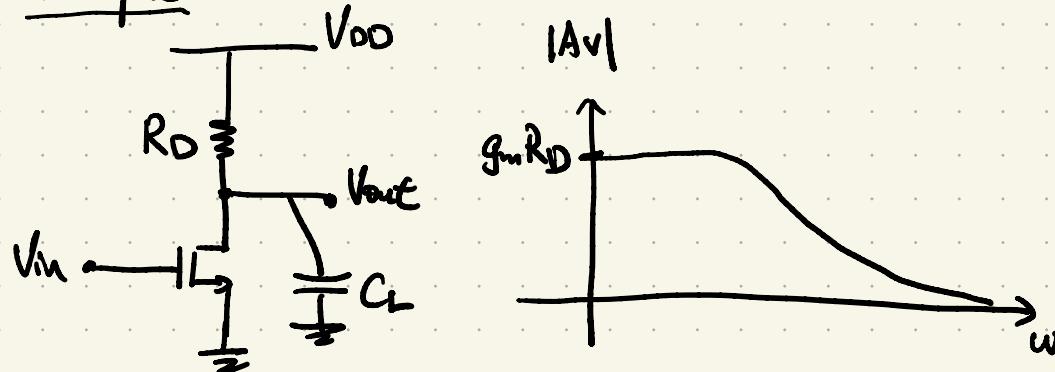


Lec 18

- Useful Frequency Response Concepts
 - Poles & Zeros
 - Bode's Rules
 - Finding Poles by Inspection

- Capacitors generally limit the BW

Example




Poles & Zeros

$$H(s) = \frac{N(s)}{D(s)}$$


↓ zeros
↓ poles

Bode's Rules

- As ω passes a pole frequency, the slope of $|H|$ decreases by -20 dB/dec

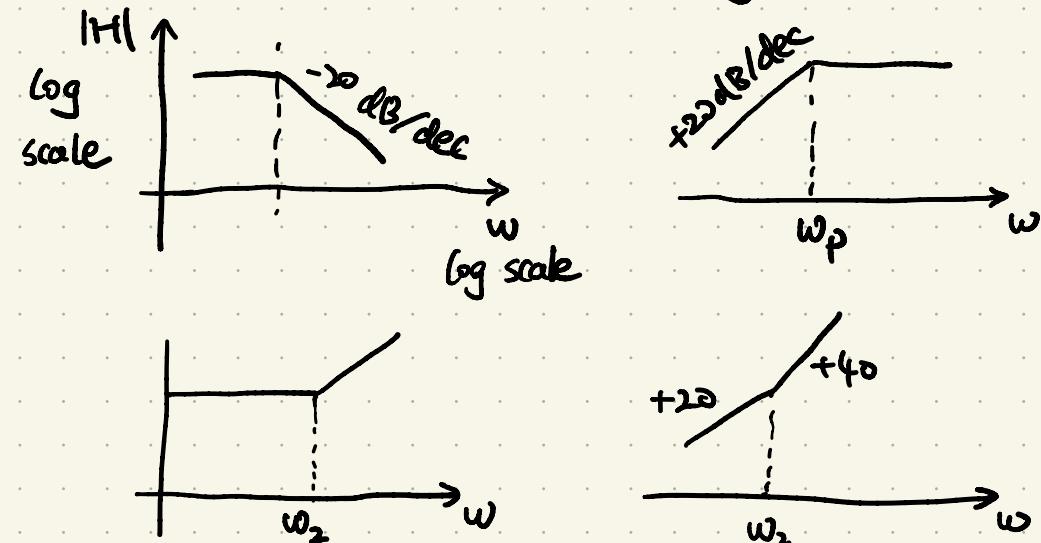

Example

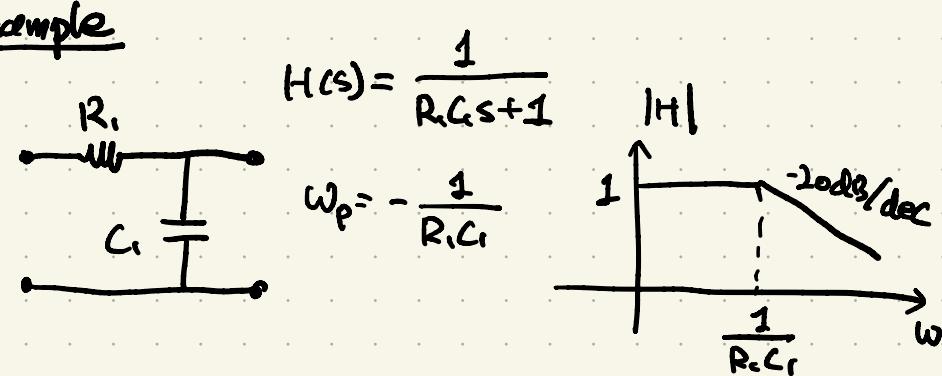


Finding Poles by Inspection

We can assume that each node in the signal path contribute a pole

To calculate the pole:

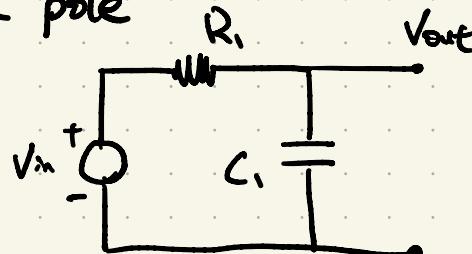(a) Find the resistance from that pole to ac GND




(b) Find the capacitances from that node to ac GND


$$\text{ac GND}$$

$$\omega_p = \frac{1}{RC}$$

all indep. sources = 0

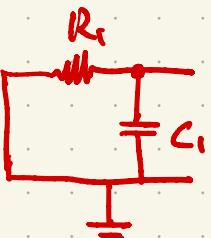


Q:

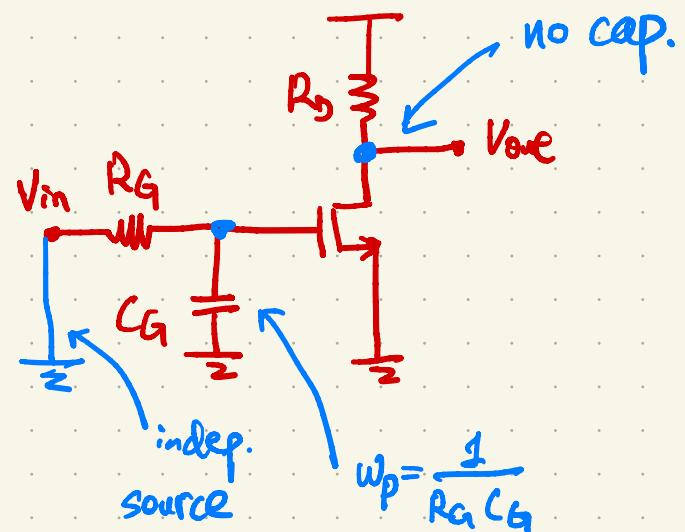

$$\omega_p = \frac{1}{R_G C_G}$$


Example

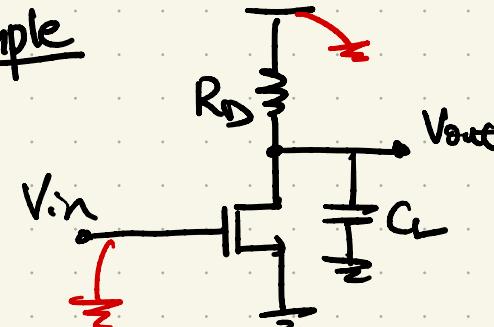

$$\omega_p = \frac{1}{R_D C_L}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_D}{1 + \frac{s}{\omega_p}} = \frac{-g_m R_D \omega_p}{s + \omega_p}$$

Example

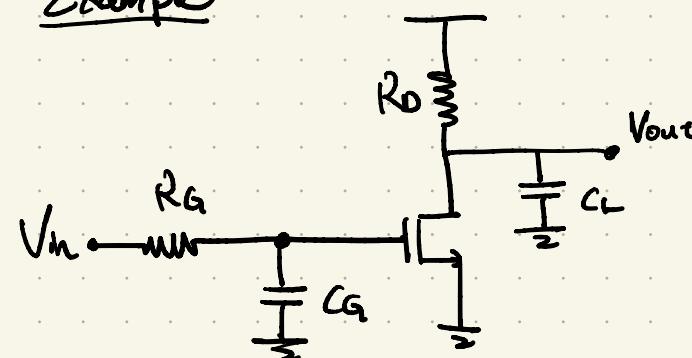


$$\omega_{p1} = \frac{1}{R_G C_G}$$

$$\omega_{p2} = \frac{1}{R_D C_L}$$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{-g_m R_D}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})} \\ &= \frac{-g_m R_D}{(1 + R_G(LS))(1 + R_D(LS))} \end{aligned}$$


Example

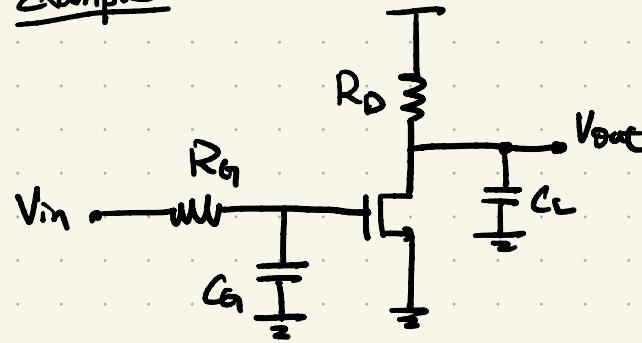


$$w_{p1} = \frac{1}{R_g C_g}$$

$$w_{p2} = \frac{1}{R_d C_L}$$

Plot the freq response

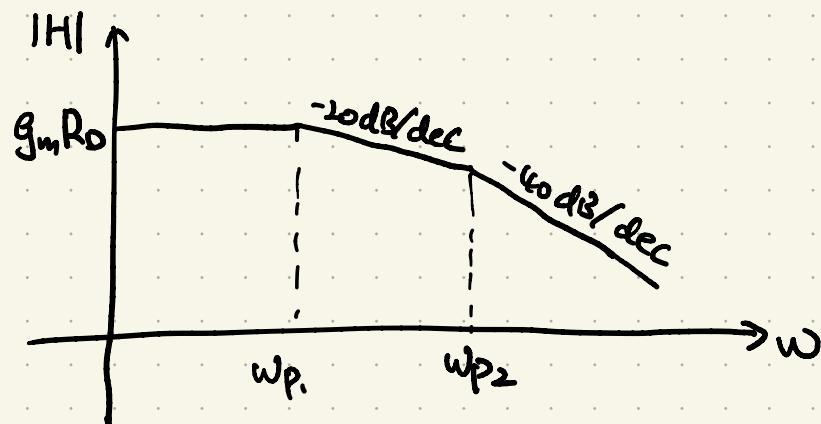

A Complication

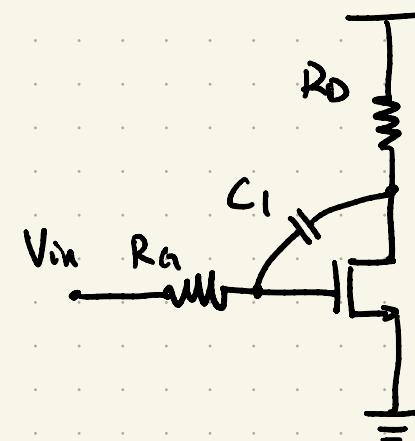

We may handle this
by Miller's theorem